
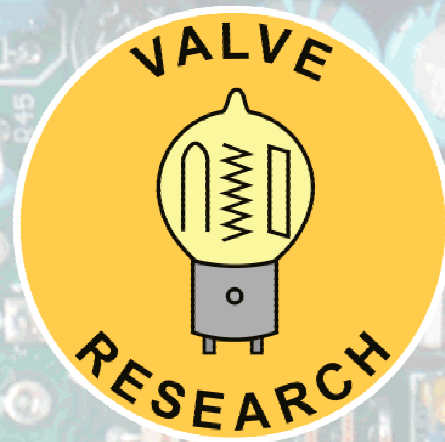

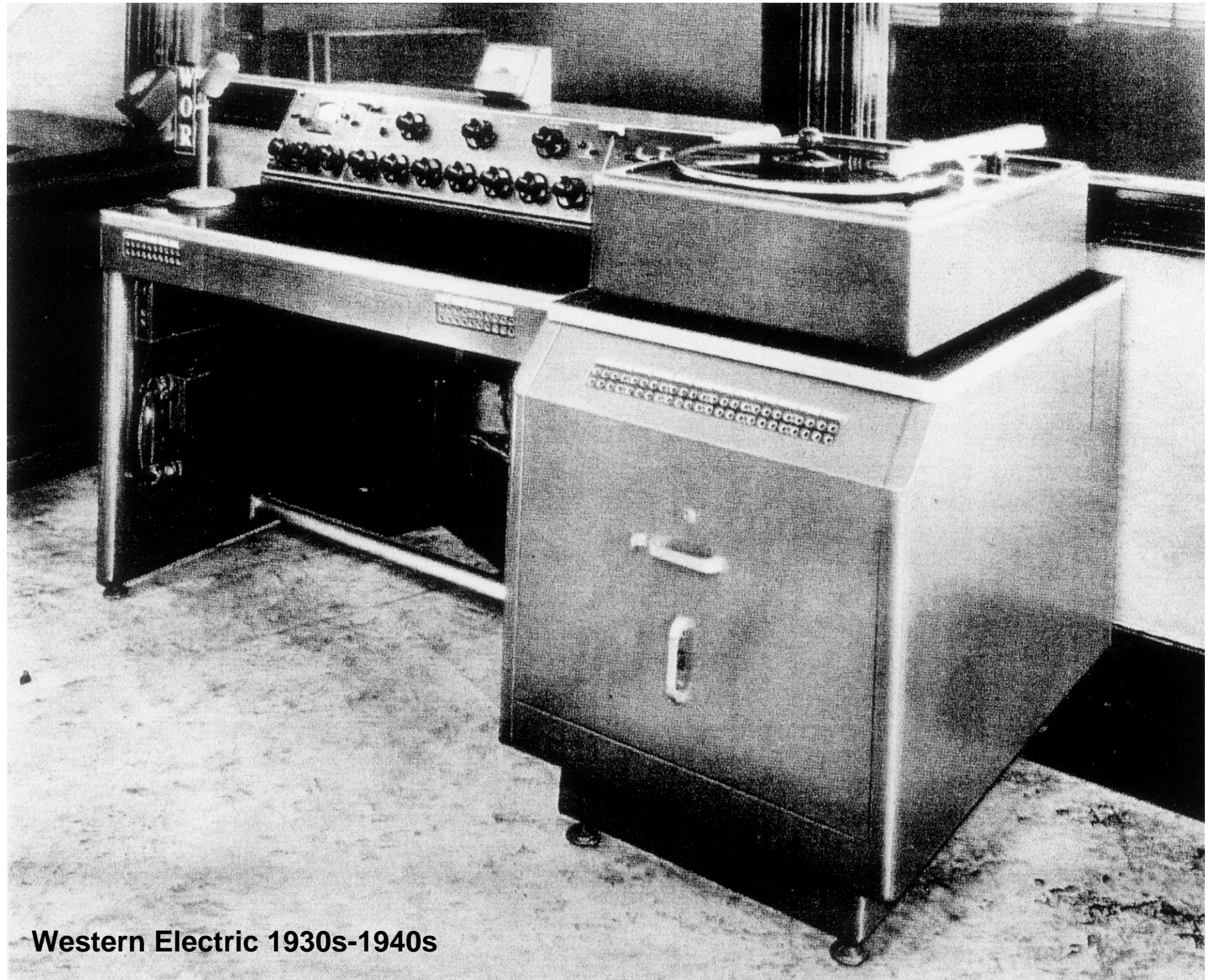
# Microphone Amplifier History and Design



Audio Engineering Society  
Adelaide Section. August 15 2006



**Graeme J Cohen**




Western Electric 1930s-1940s

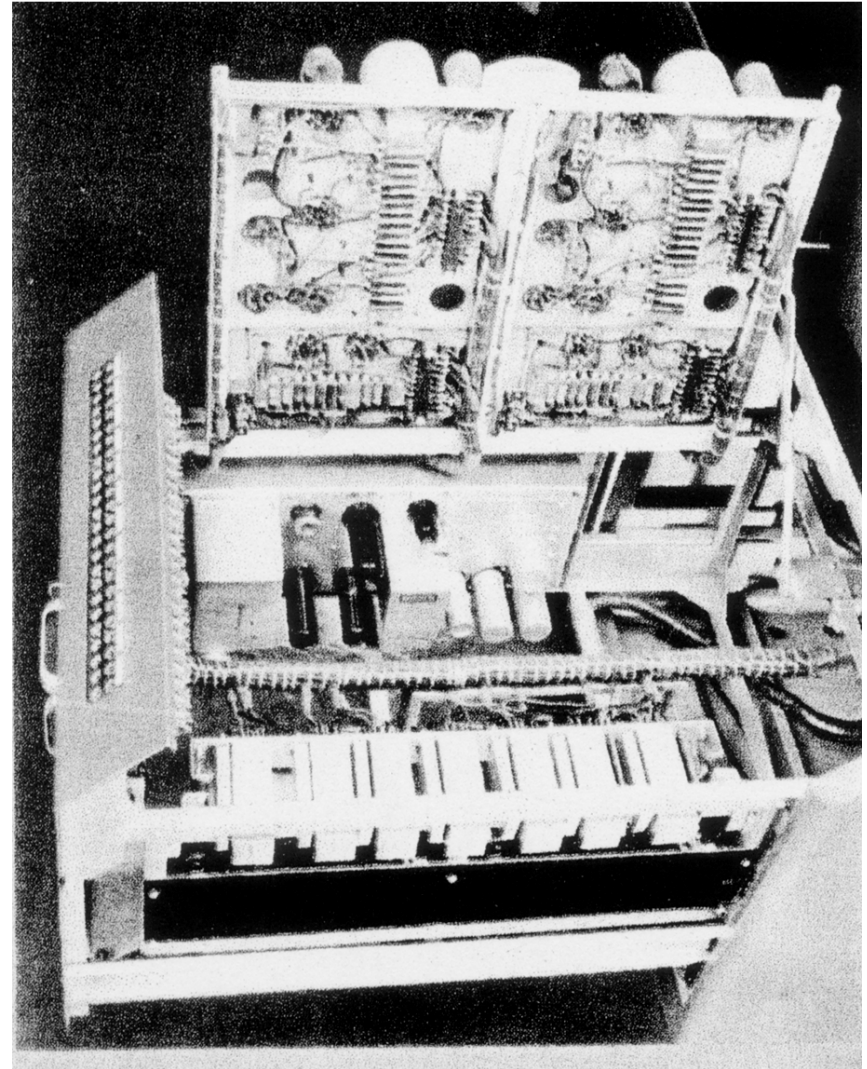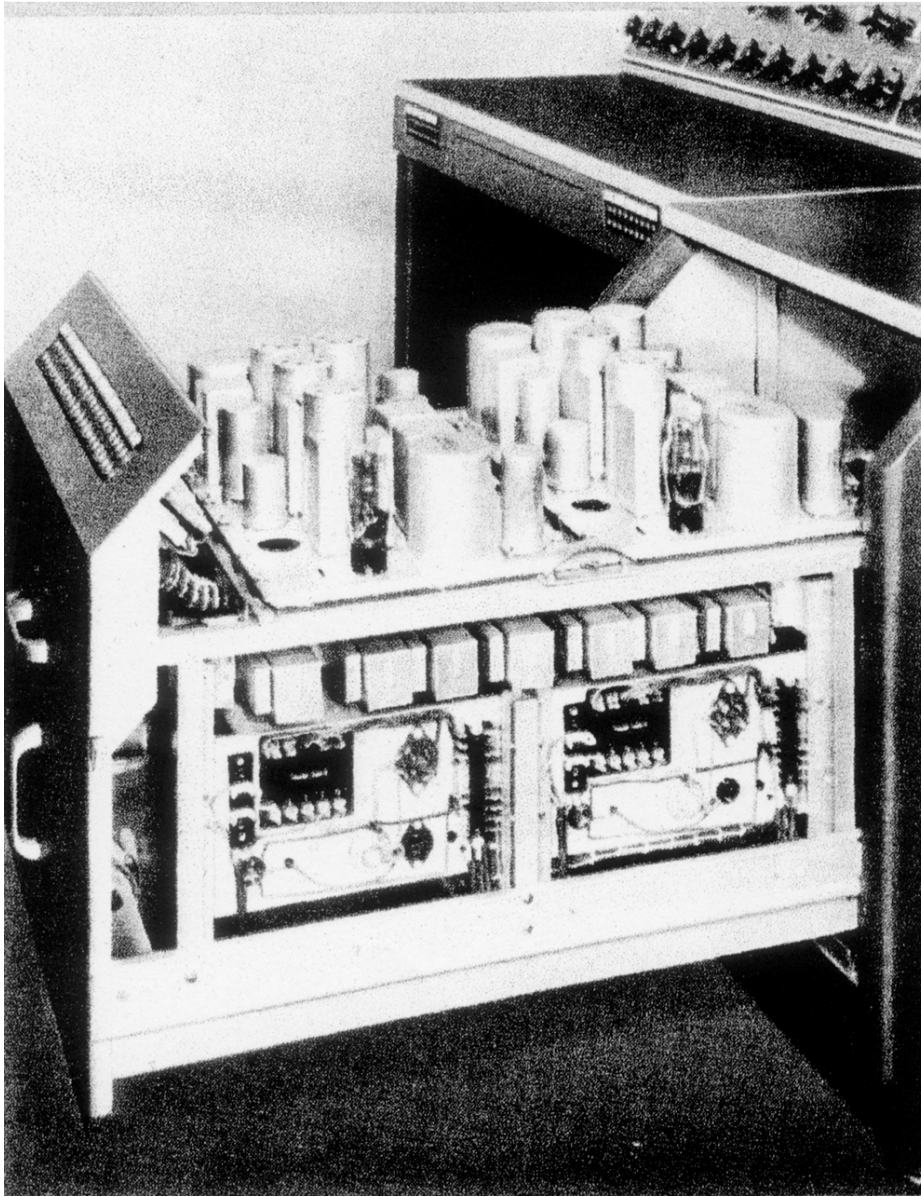


**Western Electric 1930s-1940s**



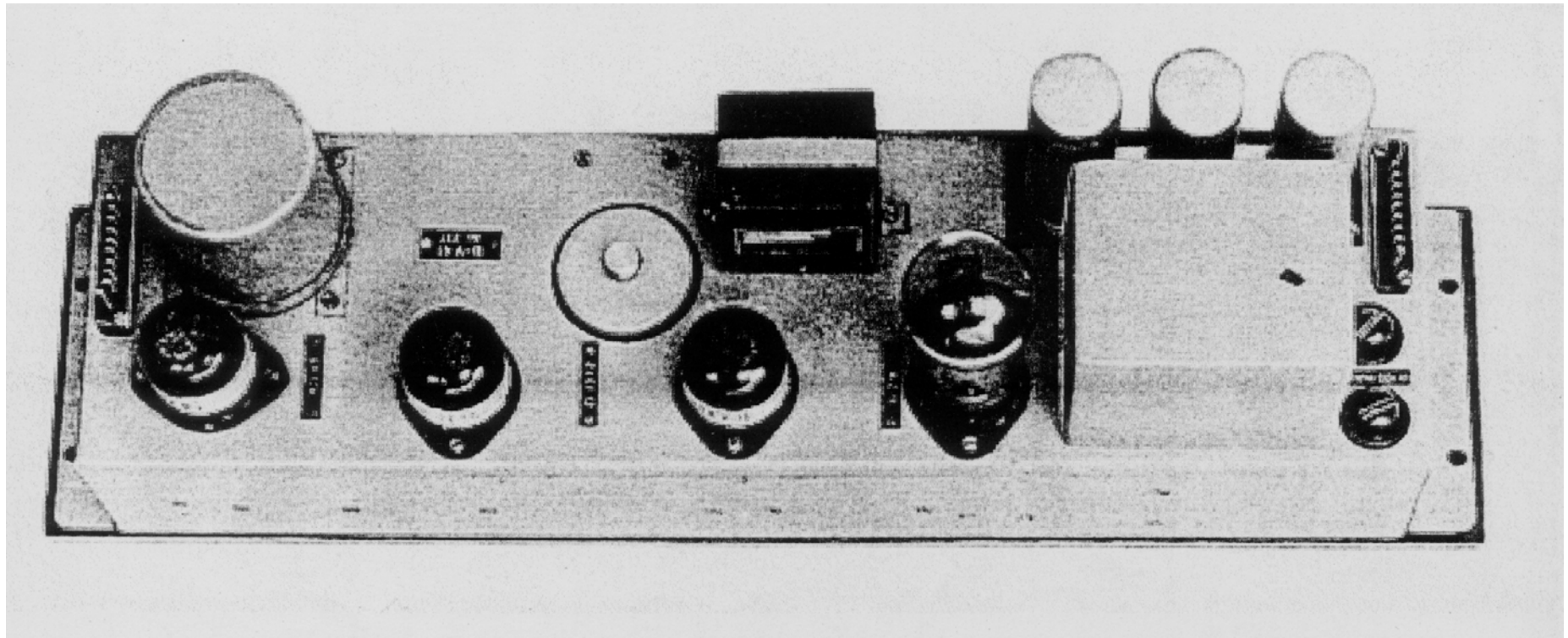

German Broadcasting 1940s

# German Broadcasting 1940s

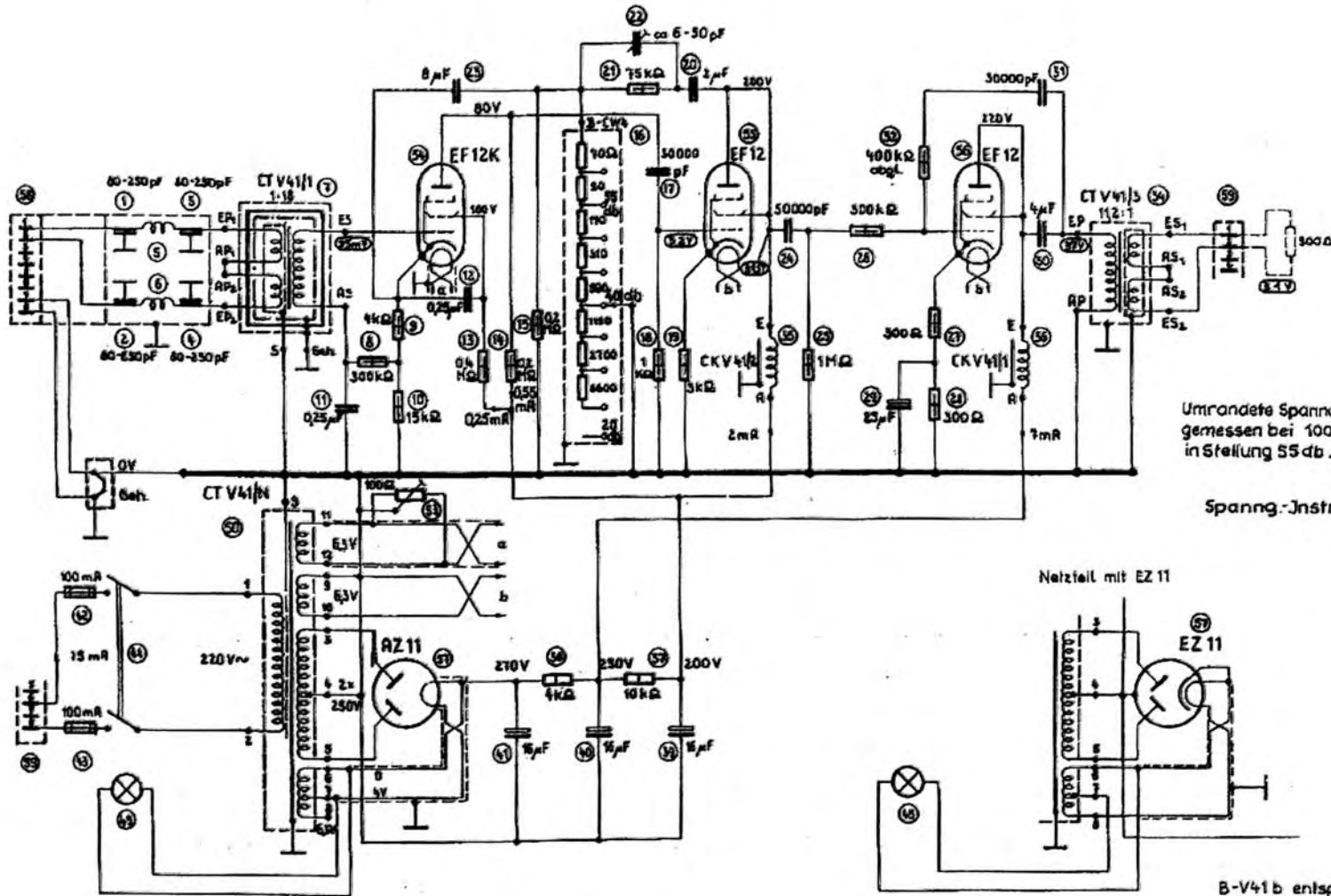


Umränderte Spannungen gemessen bei 1000 Hz in Stellung S5 db.

Spanng.-Instr. Ri ≥ 1 MΩ


Netzteil mit EZ 11

B-V41b entspricht B-V41 Ein Unterschied besteht in der mechan. Ausführung Pos 25 ist im B-V41 6 μF.


EF12 u. EF12K

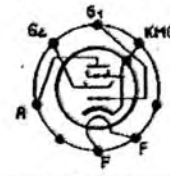

EZ 11

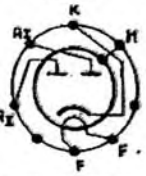

AZ 11

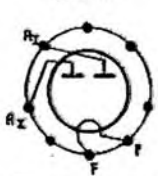

Nennspannungen der EL-Kondensatoren	
6 μF	450/500V
Pos. 28	Pos. 38, 40, 41


Nennspannungen der Kondensatoren			
125V	160V	250V	500V
Pos. 11, 31	Pos. 23	Pos. 1, 2, 3, 4	Pos. 12, 17, 20, 24, 30e

Pos. 30: MP-Kondensator, 350V Spitzenspannung 525V

Werkstoff:



Dr.-Inhalt Nr.	Chk.	289 52	M
B-V41b	Char.	270 50	
	Stand.	12.10.34	
Mikrofon- und Hauptverstärker (Neue Ausführung)			
S 473			

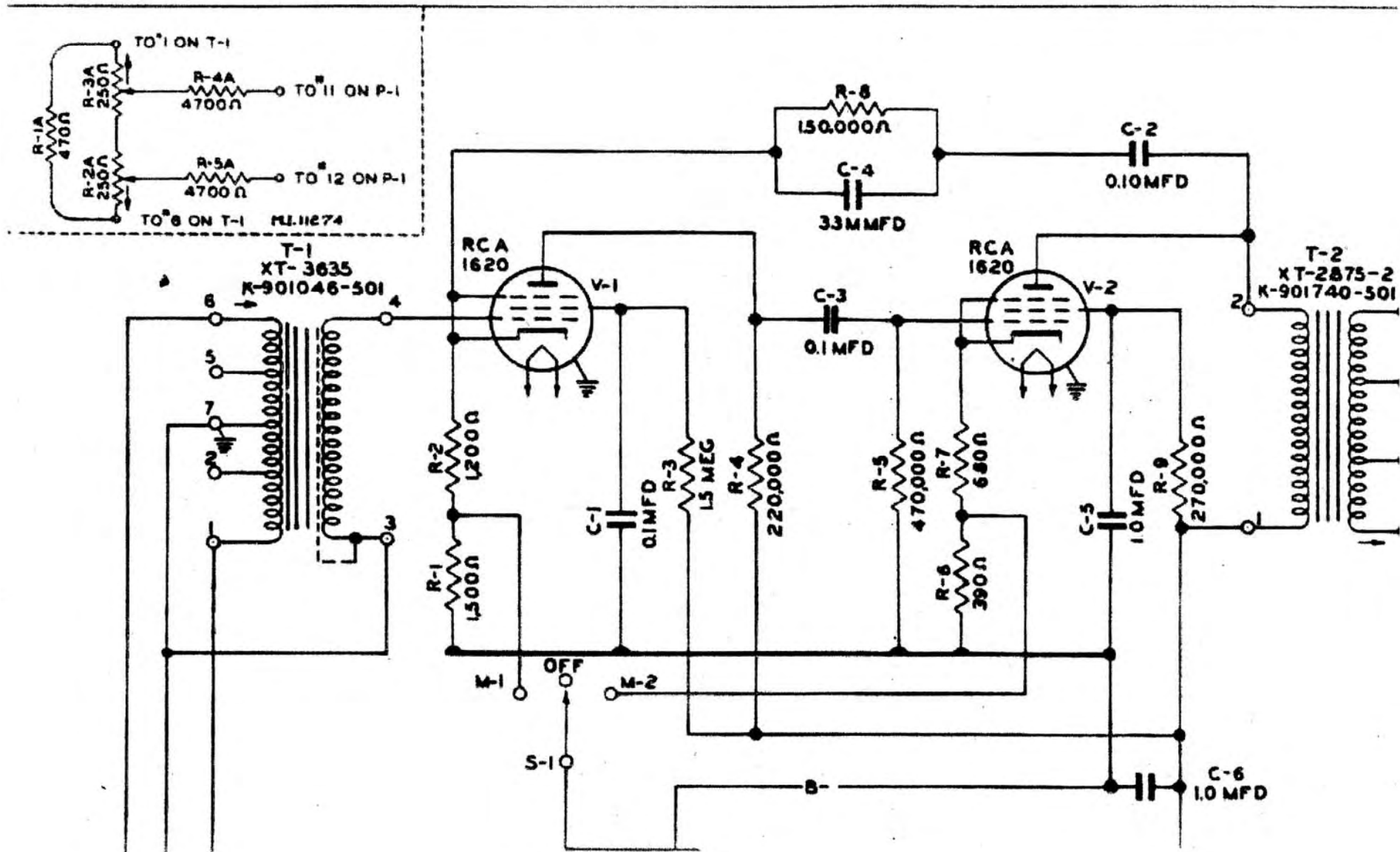


RCA BA-1A from 1945

# PLUG-IN AMPLIFIERS


BY  
*Langevin*

TYPE 116-B... TYPE 117-A

*Complete Plug-In Audio Facilities  
with Only 2 Types of Amplifiers  
2 Types of Vacuum Tubes*

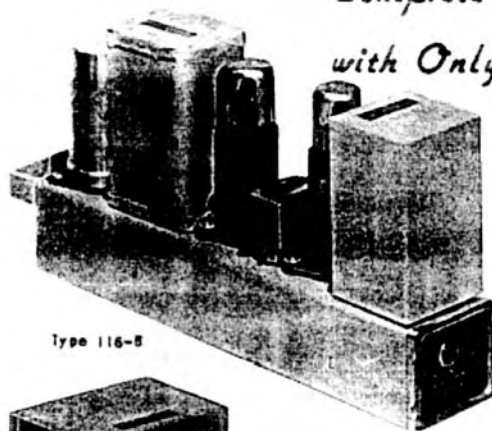

Type 116-B

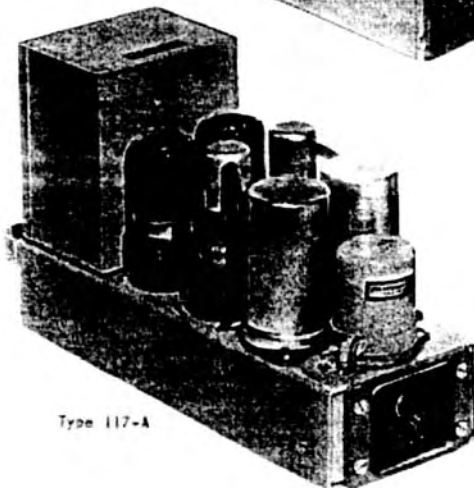

Type 117-A

- STUDIOS STAY IN SERVICE
- LOWER OPERATING COST
- LOWER MAINTENANCE COST
- LOWER INVENTORIES
- RACK SPACE-SAVERS
- AMPLIFIERS EXCEED FCC QUALITY REQUIREMENTS FOR FM
- AMPLIFIERS PROVIDE HIGH OVERLOAD SAFETY FACTOR


1940s - 1950s

MAXSON INSTRUMENT CORP. • LONG ISLAND CITY, N.Y.  
The equipment herein described is licensed under U.S. patents of the A.T.&T. Co. and the Western Electric Company


*Langevin*





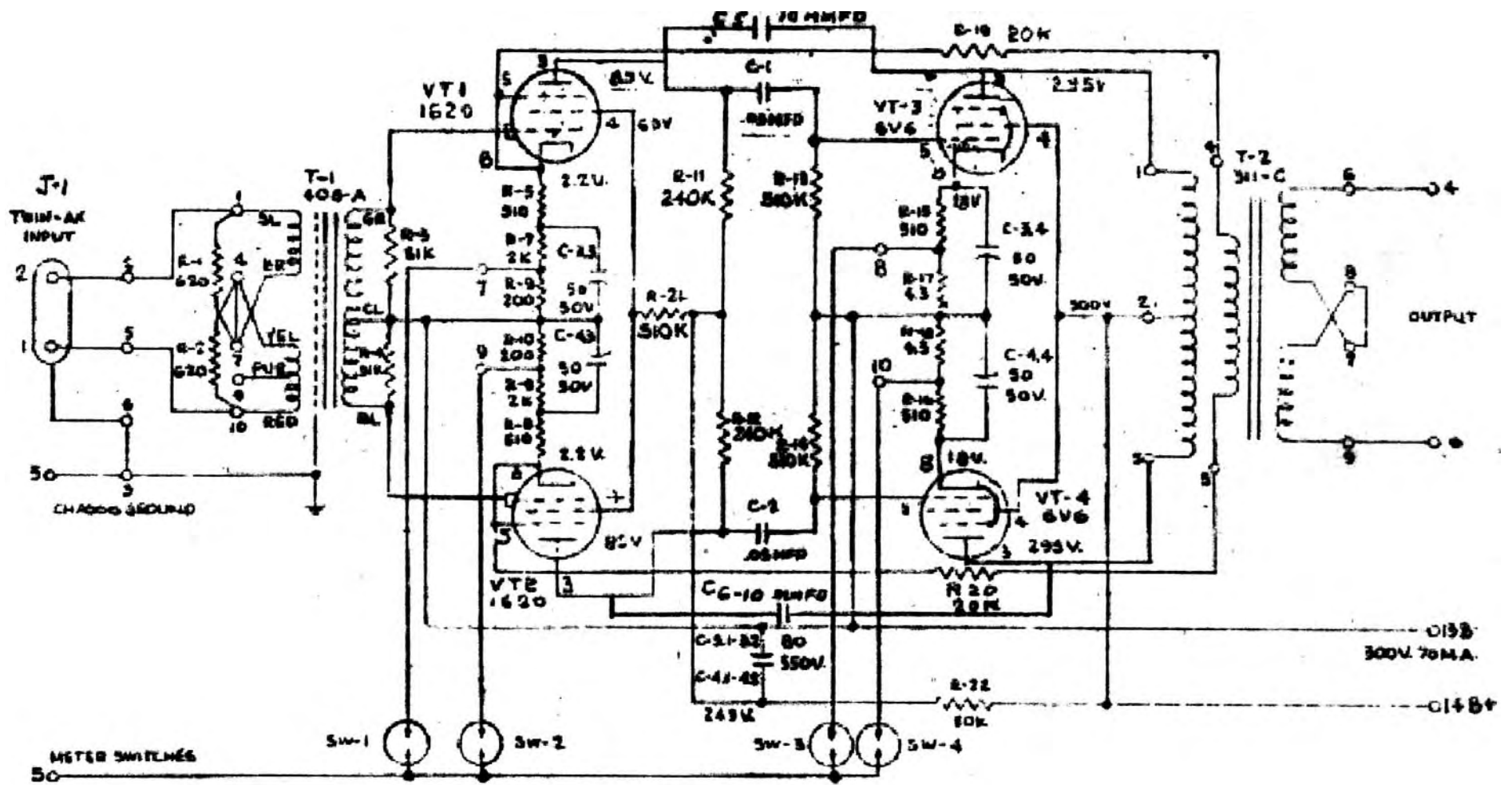

Langevin 1947

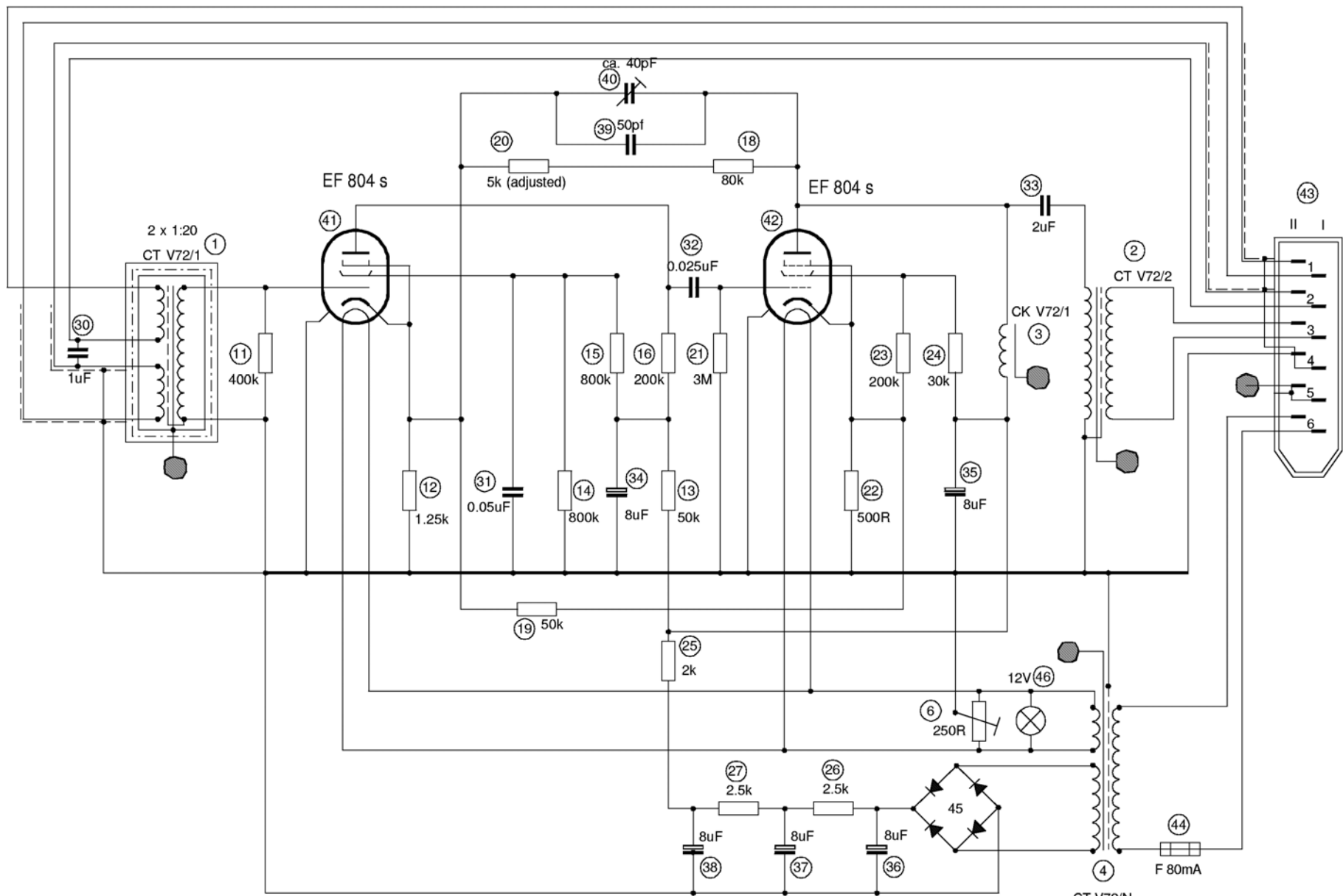


Position	Volt	Type
39	500V	Keramik
30	3V~	Papierkond.
31;32	250V	Papierkond.
33	250V	MP-Kond.
34 ;35 ;36 ;37 ;38	450V	Elkos

**Siemens & Halske 1952**

<p><b>Studioverstaerker V72</b>          Siemens &amp; Halske A.G.          Nach einer Entwicklung des NWDR          Date of original diagram: 30.8.52</p>	<p>redrawn by:  </p>
--	--------------------------

from Serial No. 1001

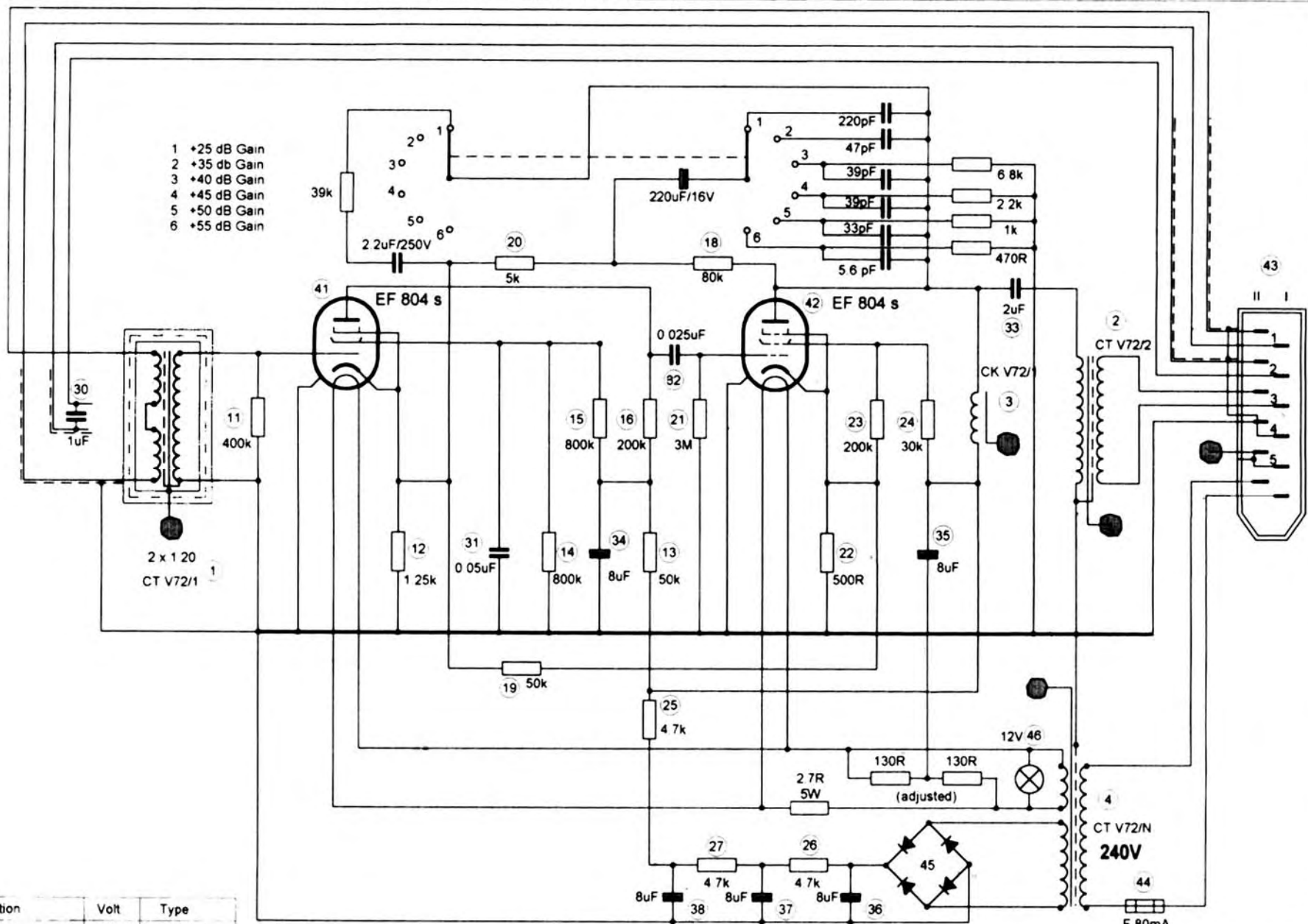

- 1 +25 dB Gain
- 2 +35 dB Gain
- 3 +40 dB Gain
- 4 +45 dB Gain
- 5 +50 dB Gain
- 6 +55 dB Gain

Position	Volt	Type
39	500V	Keramik
30	3V~	Papierkond
31,32	250V	Papierkond
33	250V	MP-Kond
34,35,36,37,38	450V	Elkos

**Siemens & Halske 1952**  
**Modified by G J Cohen 1996**



**V72 +55dB Preamp (240V)**  
 Siemens & Halske A.G. Nach einer Entwicklung des NWDR  
 Modification by G J Cohen & G Wagner 1996

**supersonic**  
 COMMUNICATIONS  
AM/FM - 8100MHz - 100 MHz - 0.1MHz - 100kHz - 0.1kHz

März 1962

# Studio Verstärker V 72 a

A IV, 60-1

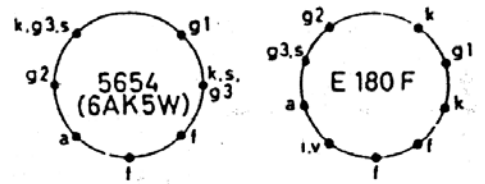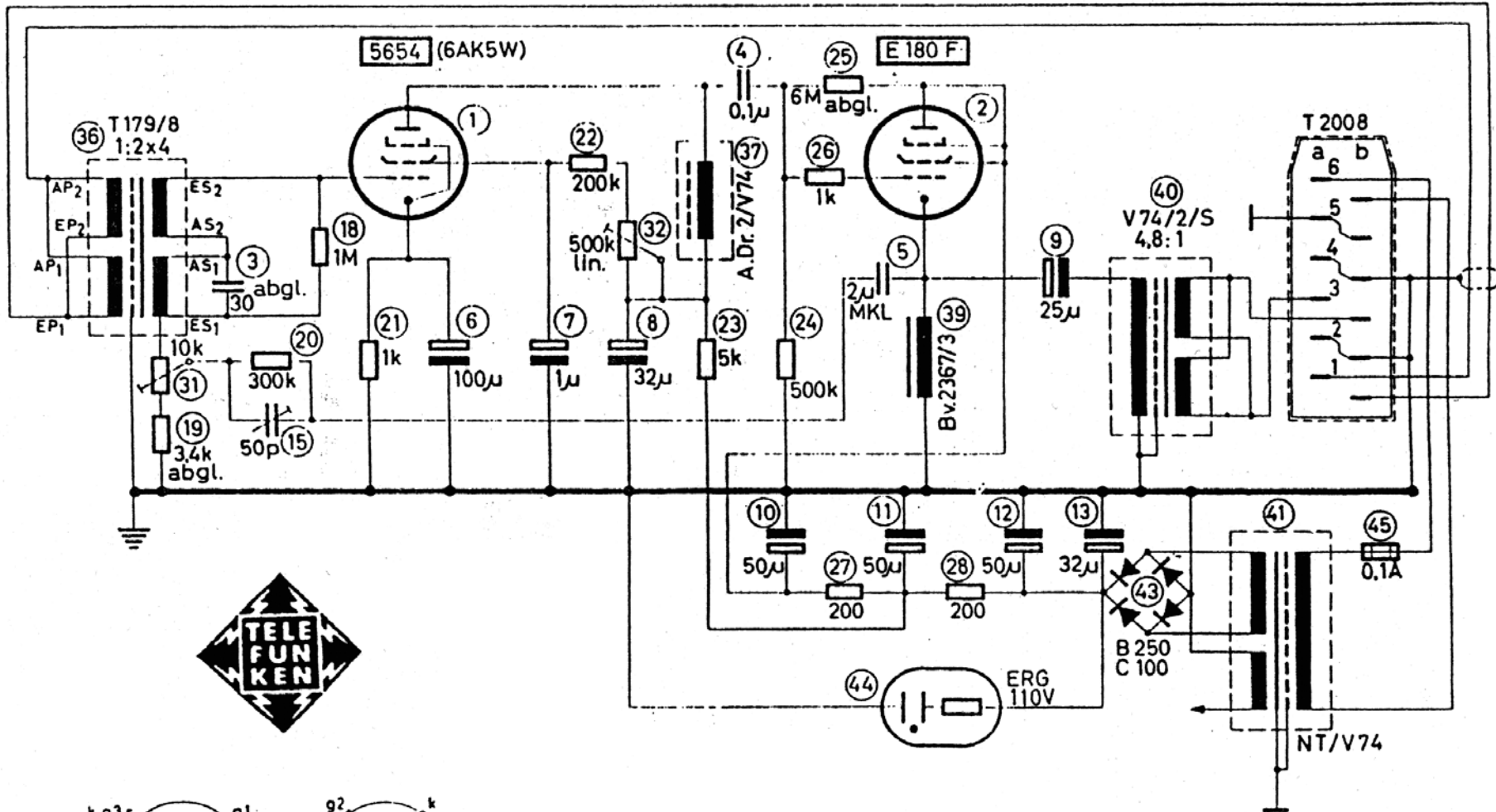

Blockierungsstellung 1 (wie V 72)

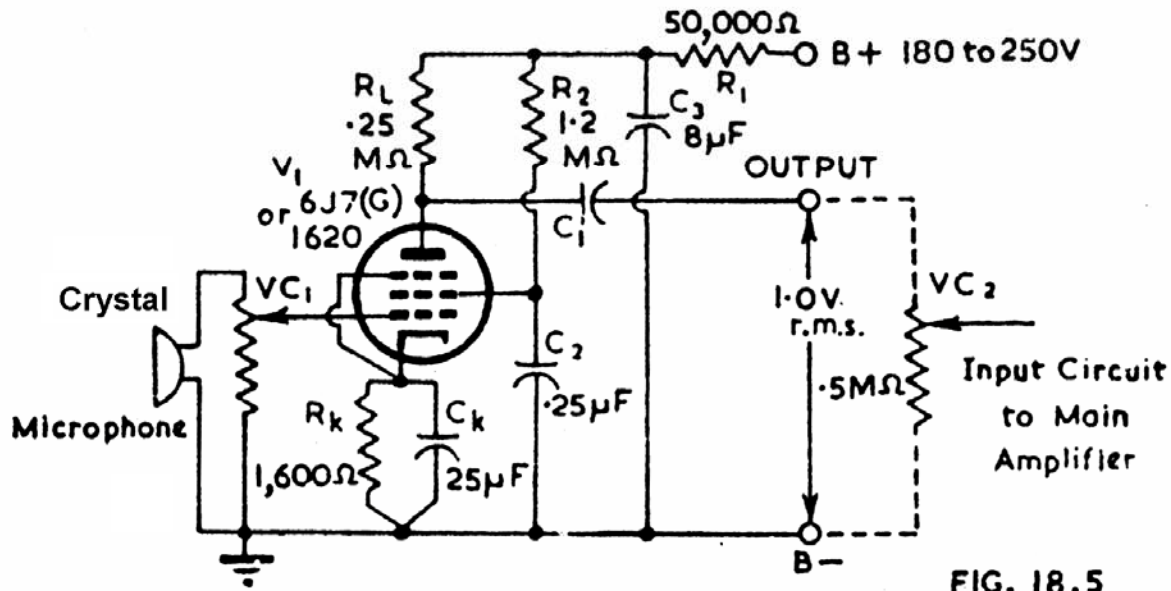


FIG. 18.5

*Fig. 18.5. Single stage pentode pre-amplifier for use with diaphragm-type crystal microphone.*

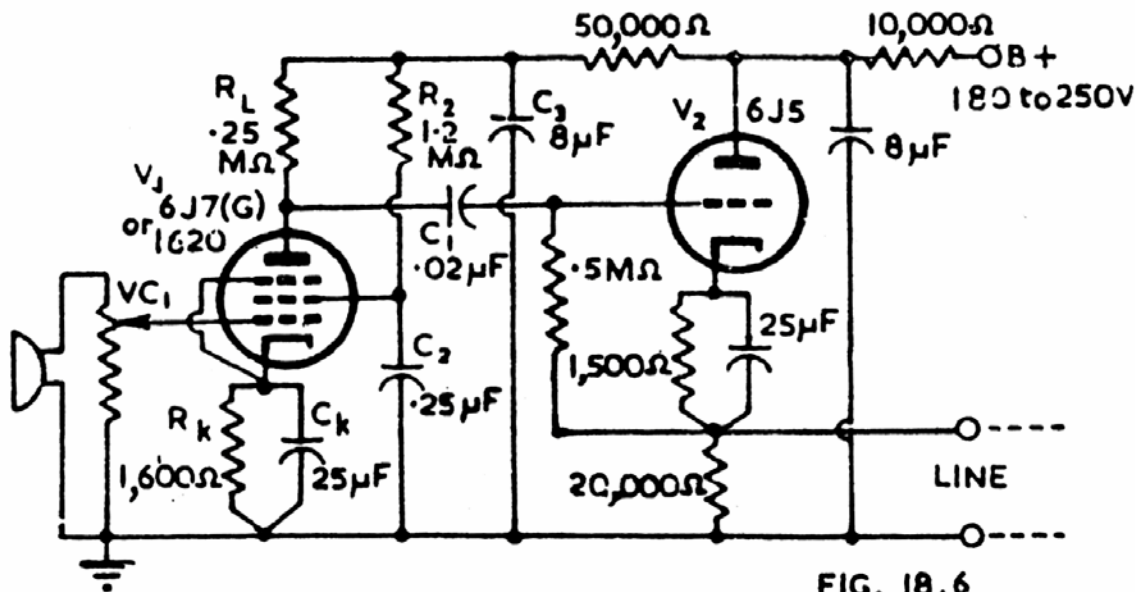


FIG. 18.6

*Fig. 18.6. Single stage pentode pre-amplifier followed by cathode follower, for use with diaphragm-type crystal microphone.*

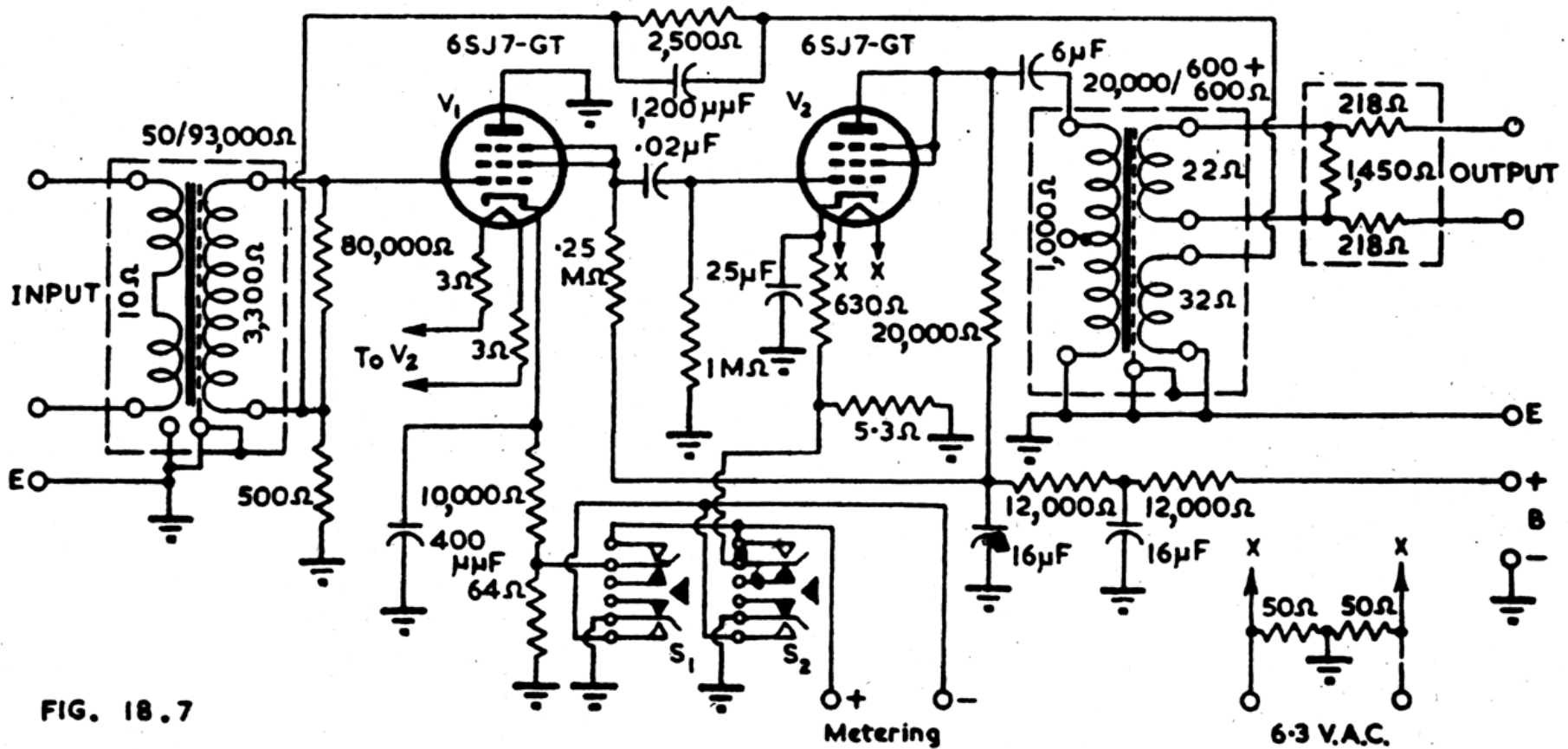


FIG. 18.7

Fig. 18.7. Two stage broadcast station microphone pre-amplifier with gain of 29 db.

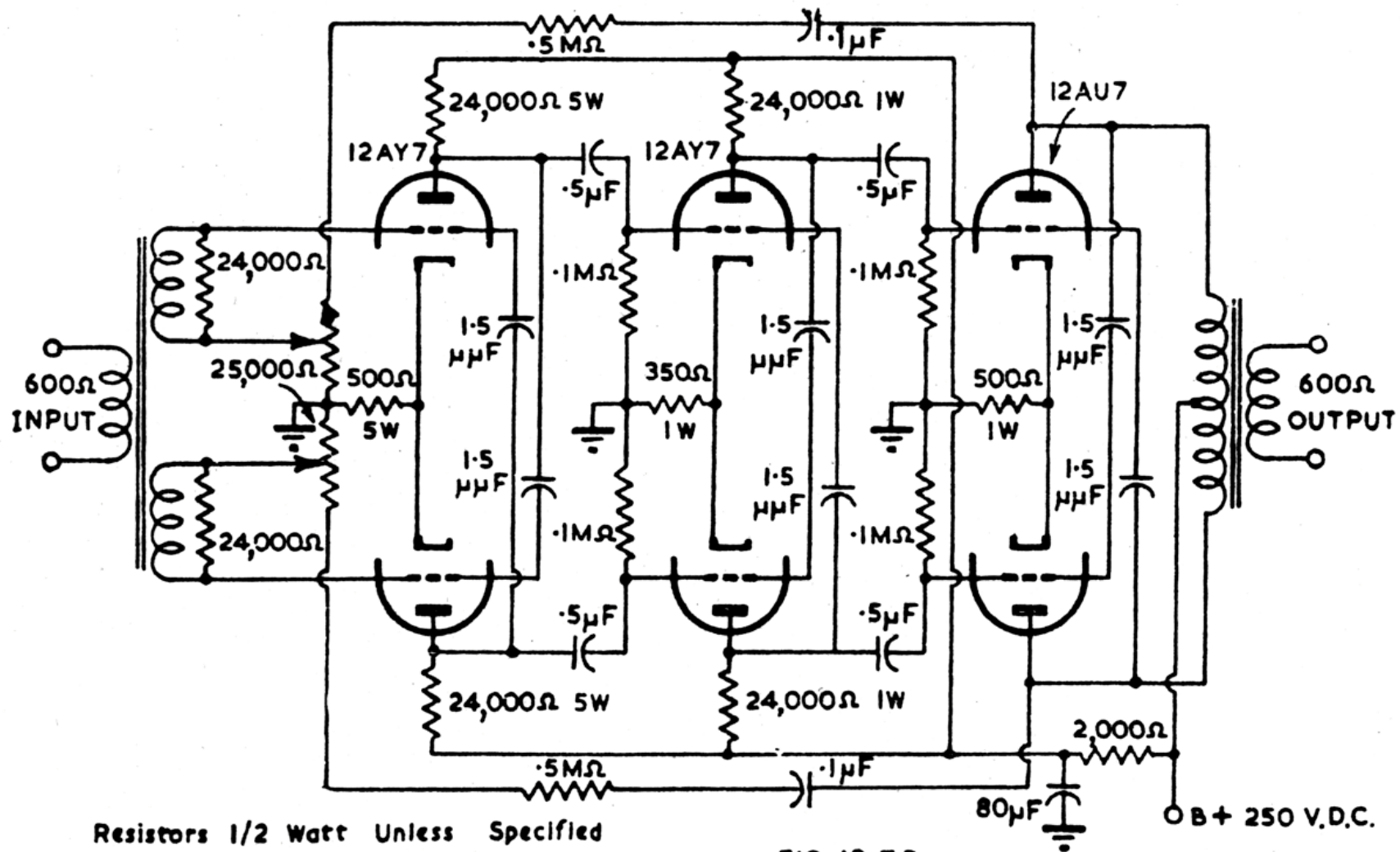


FIG. 18.7 B


Fig. 18.7B. Three-stage balanced cross-neutralized pre-amplifier using two 12AY7 valves and 12AU7 (Ref. B17).



AWA Consolette.

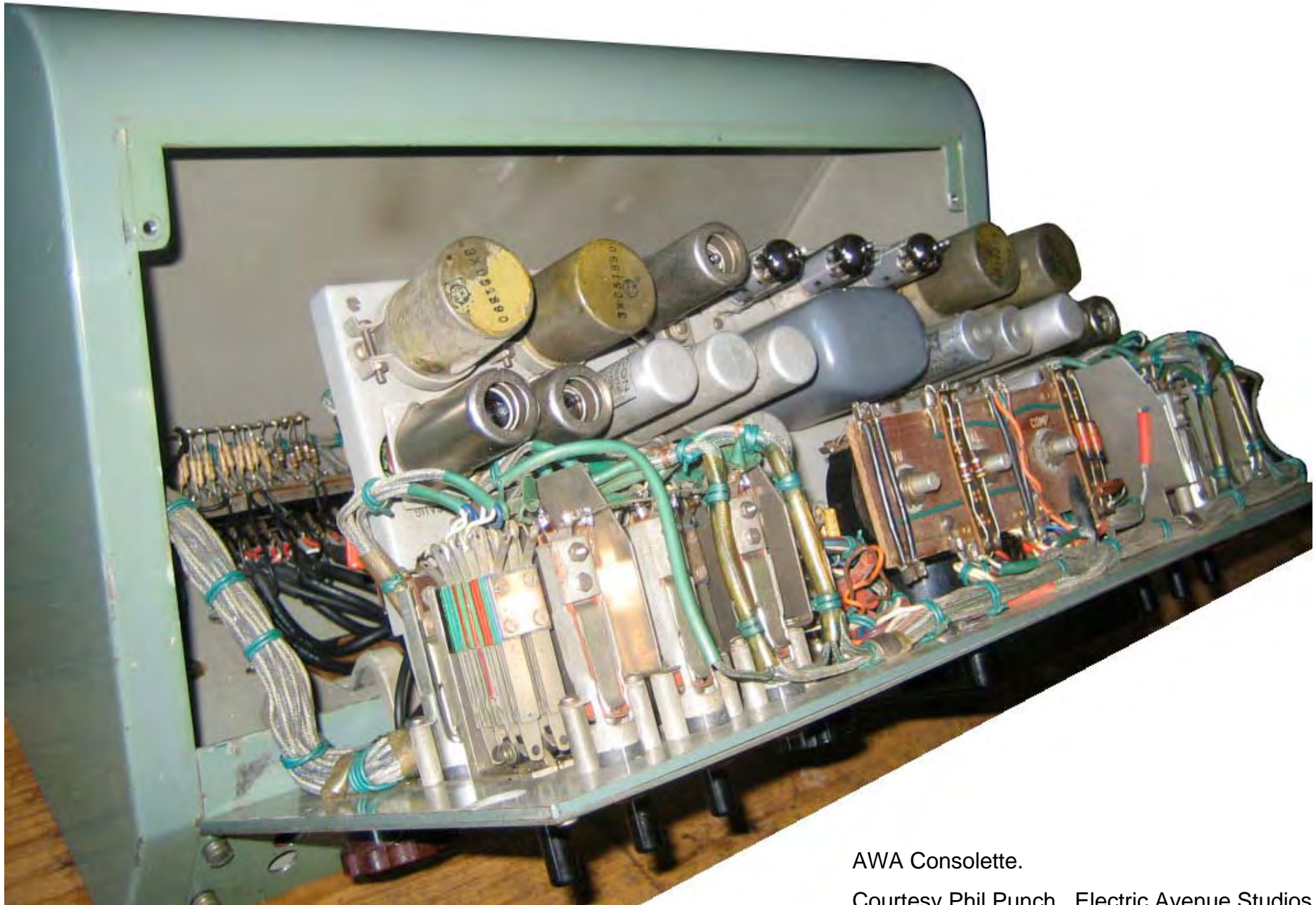Courtesy Phil Punch, Electric Avenue Studios





AWA Consolette.

Courtesy Phil Punch, Electric Avenue Studios


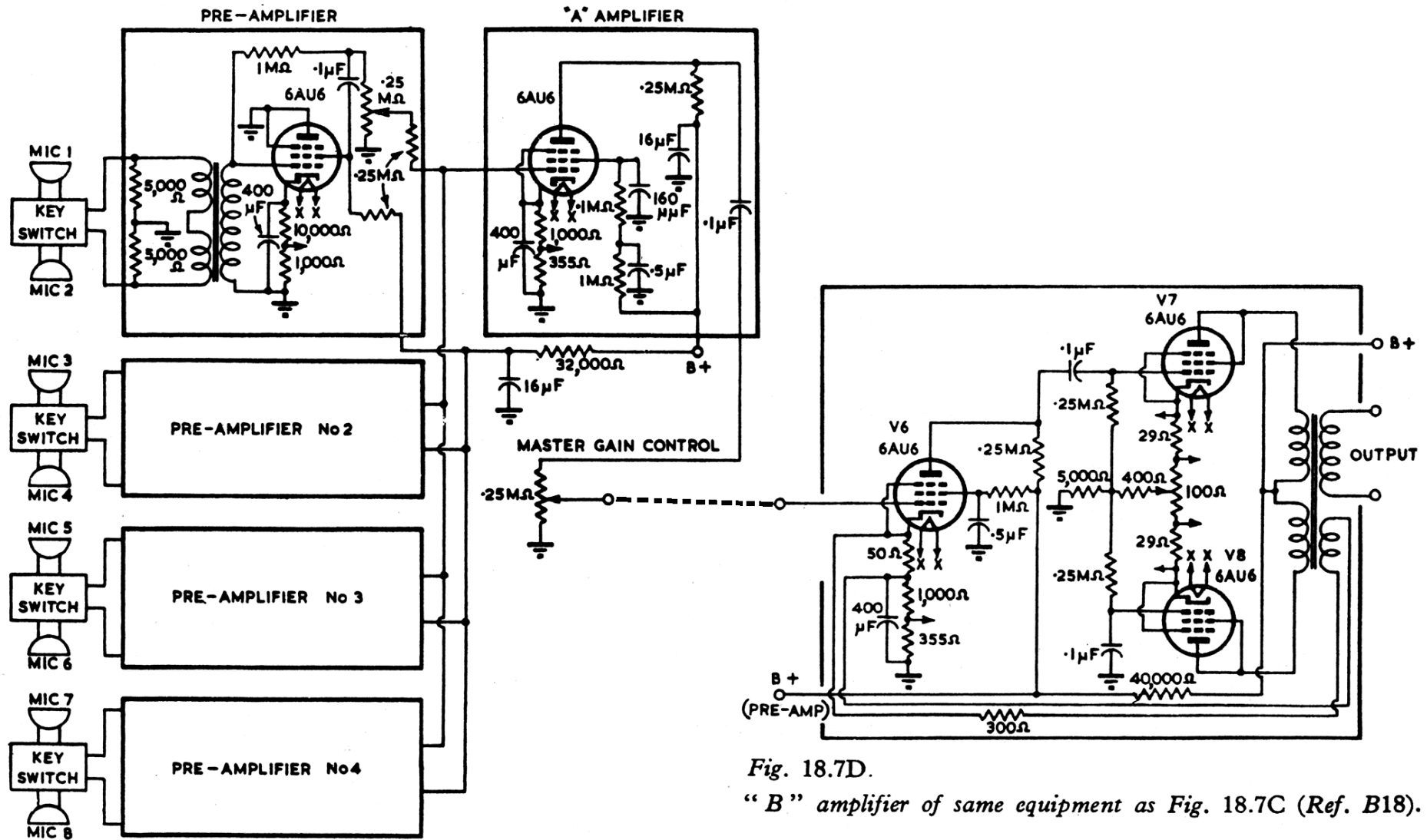


Fig. 18.7C. Essential amplifying and attenuating circuits of pre-amplifiers and "A" amplifier of single unit equipment for studio use (Ref. B18). See also Fig. 18.7D.

Fig. 18.7D. "B" amplifier of same equipment as Fig. 18.7C (Ref. B18).

**Altec M11 system 1950**

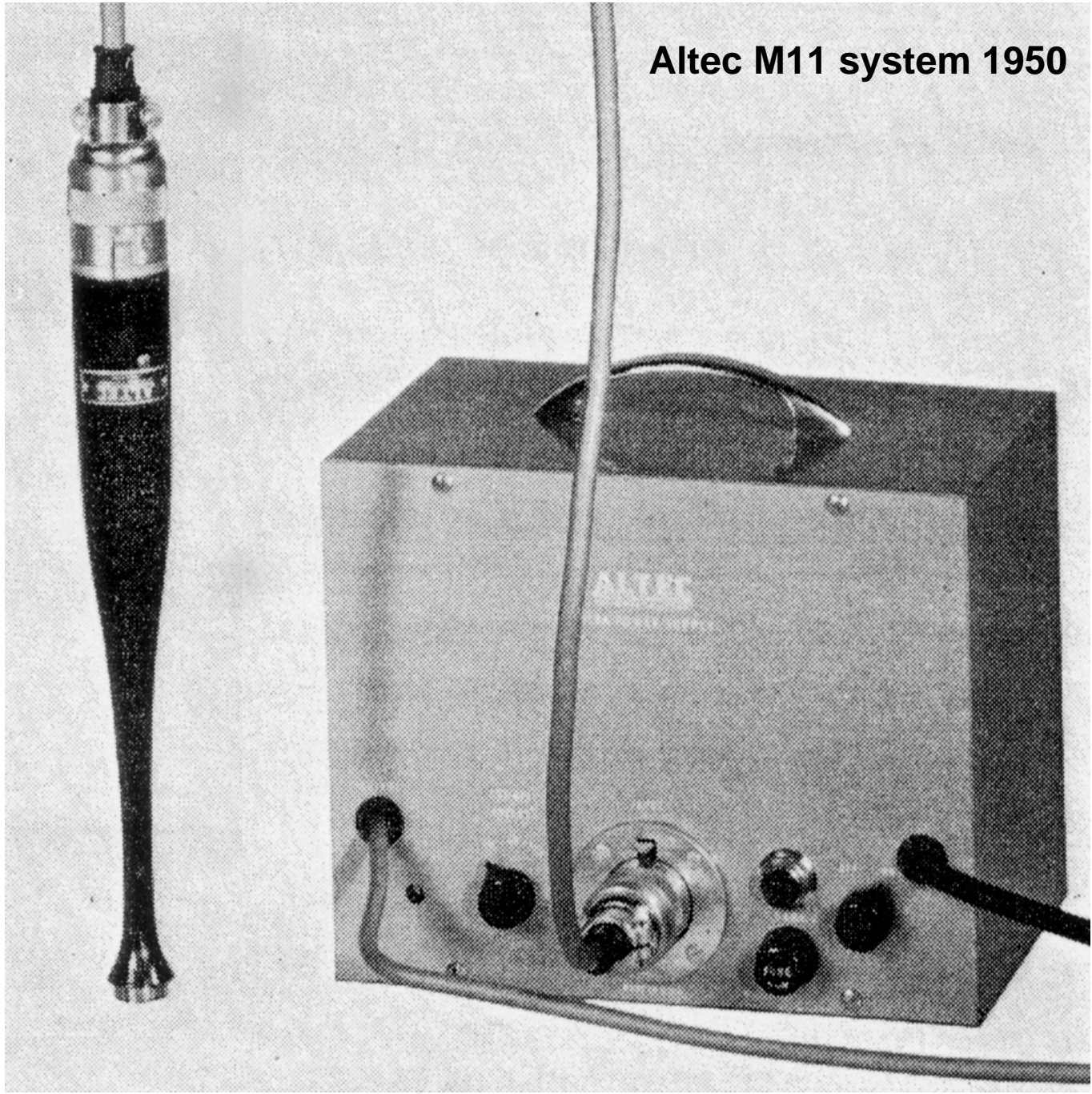

# Altec M11 system 1950

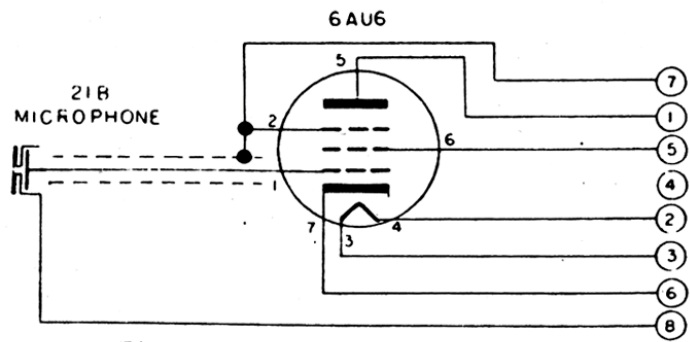


Fig. 4. 150A microphone base.


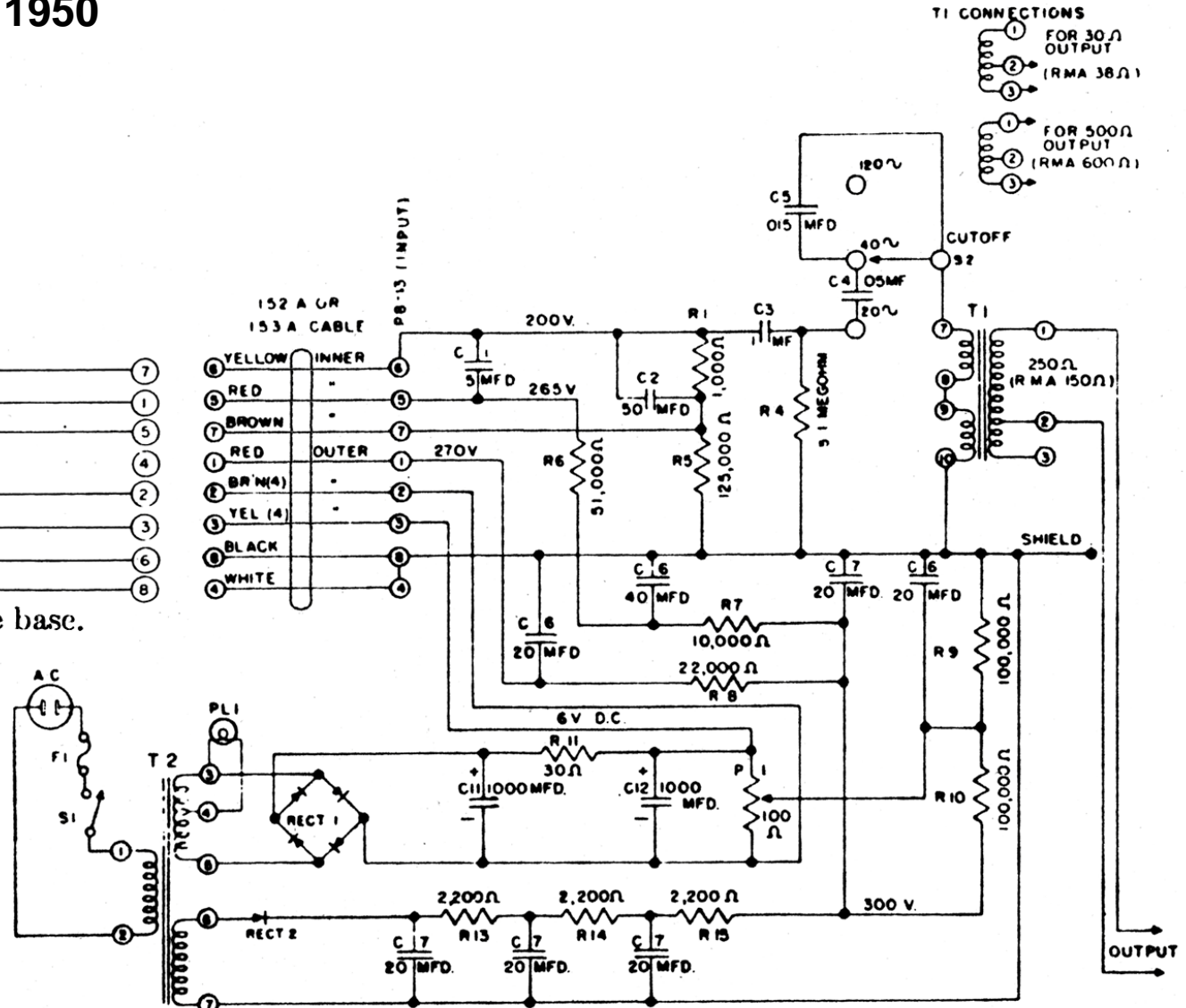


Fig. 6. P-518 power supply.

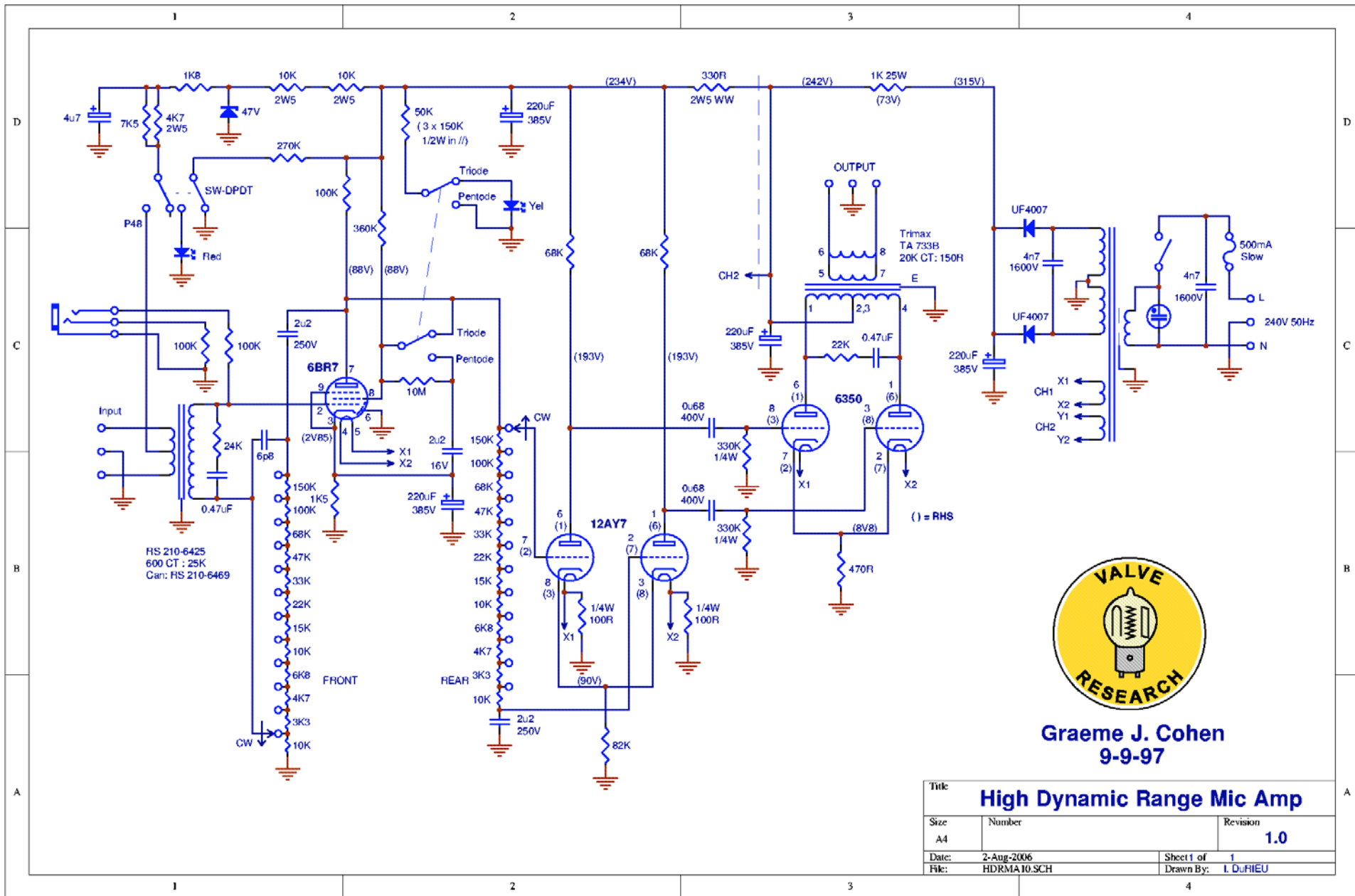

Graeme J. Cohen  
9-9-97

Title			
<b>High Dynamic Range Mic Amp</b>			
Size	Number	Revision	
A4		<b>1.0</b>	
Date:	2-Aug-2006	Sheet 1 of	1
File:	HDRMA10.SCH	Drawn By:	I. DuRIEU


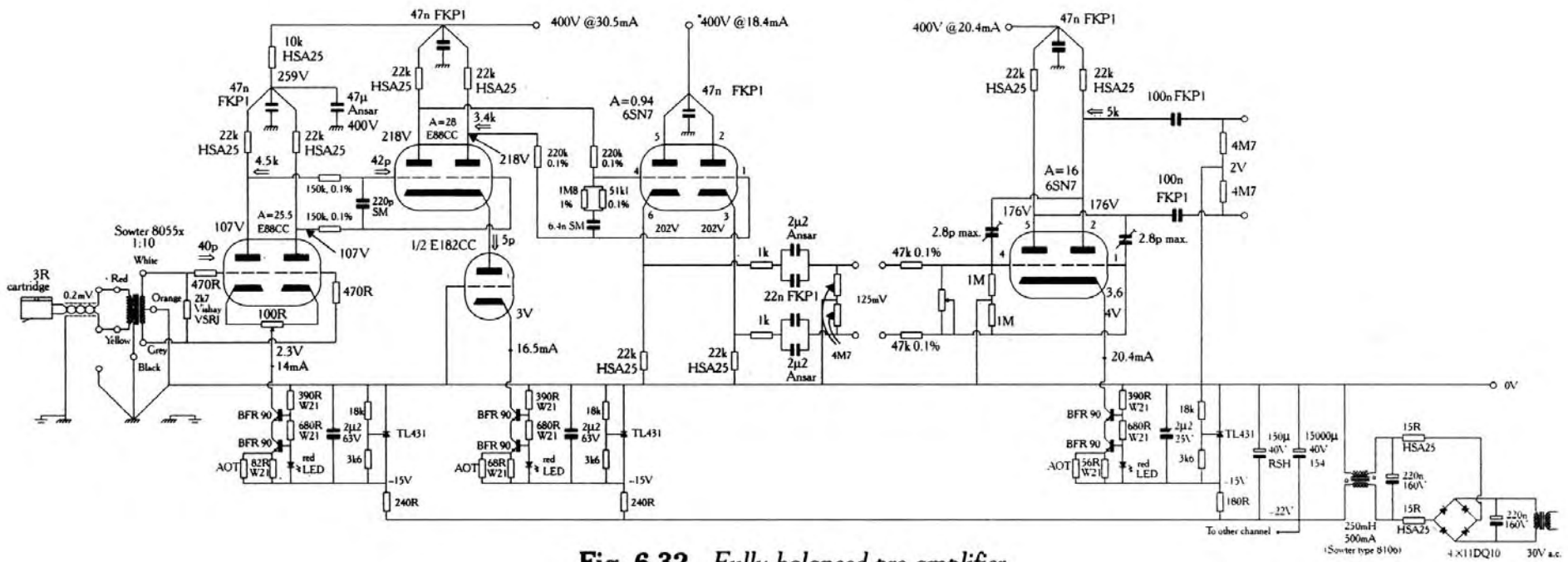


Fig. 6.32 Fully-balanced pre-amplifier

Morgan Jones 1995

# AKG C24 microphone

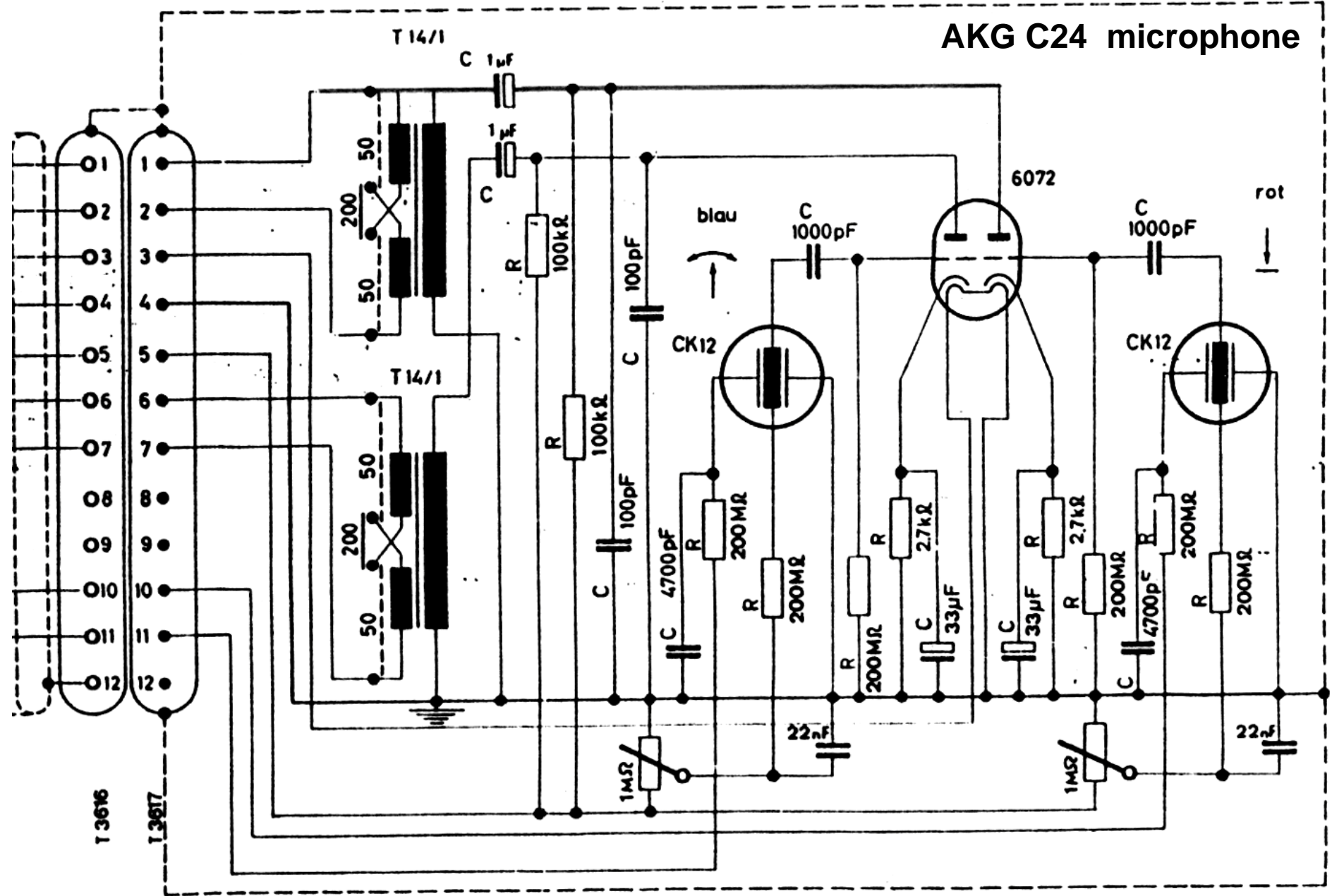


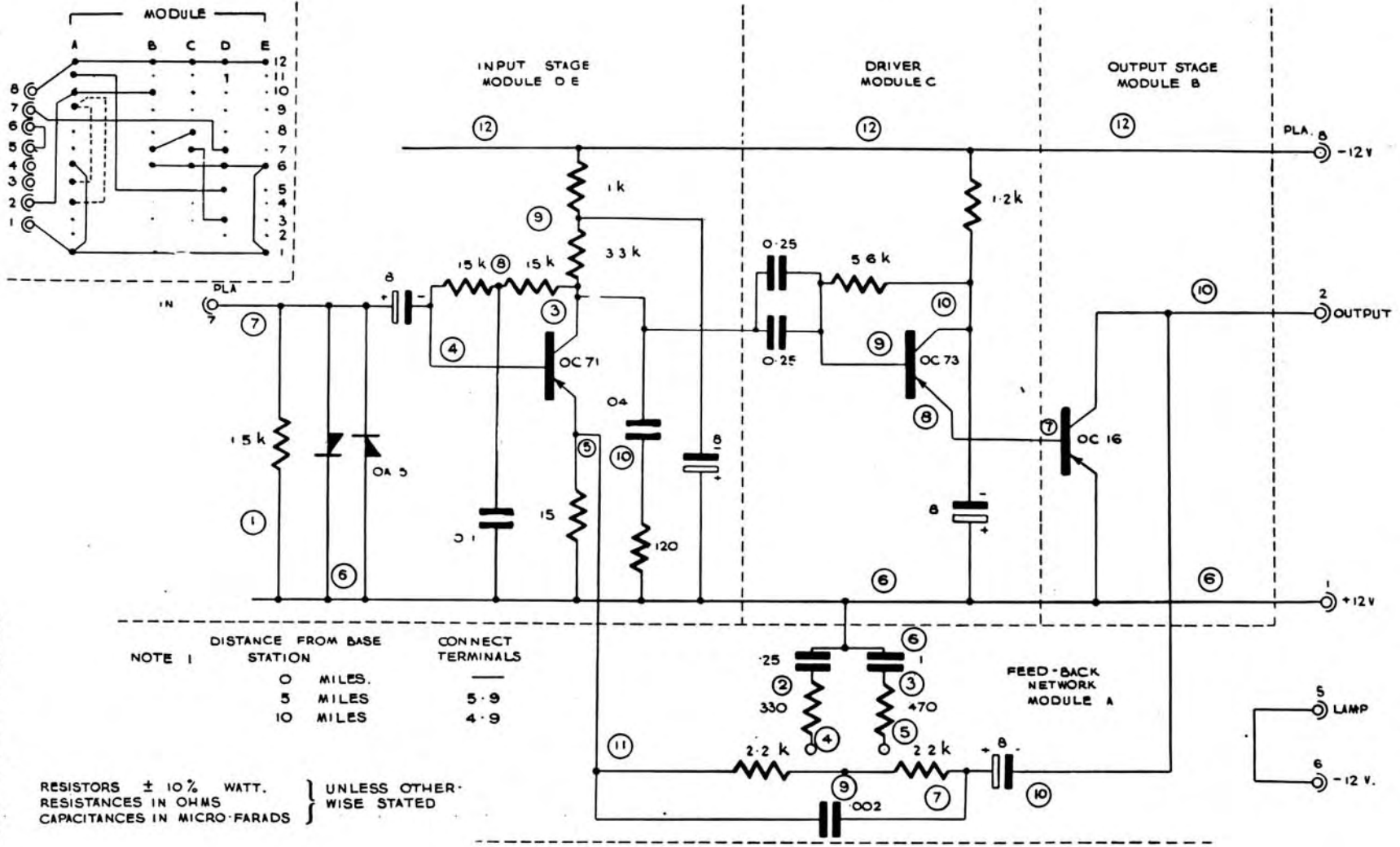


Figure 33.—Circuit diagram of intercommunication amplifier plug-in unit.

Treharne 1958

TSP. 25 DRAWN FROM C2405

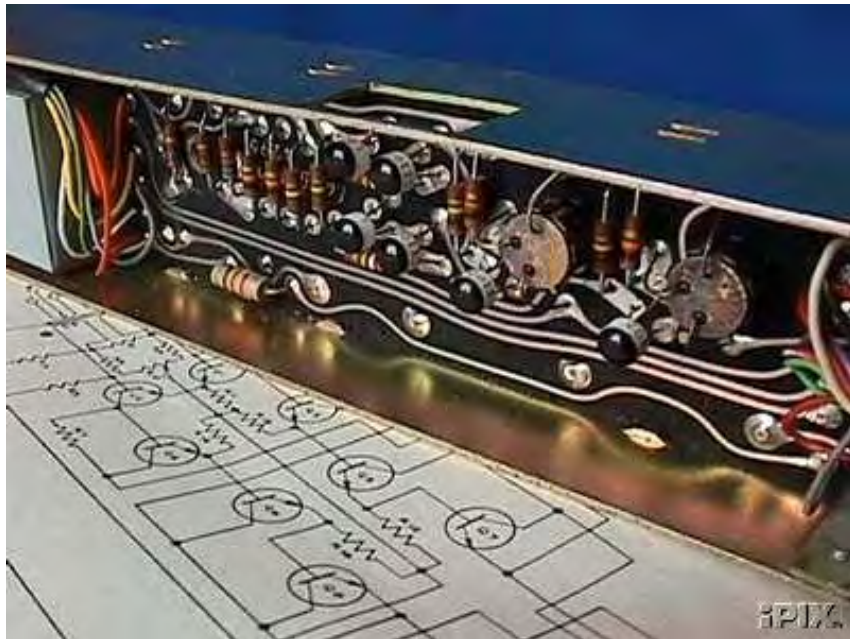




### Langevin AM16 1961

John Hall is credited with this design, and he subsequently left Langevin and went to Altec where his name can be found on the similar PP 9470A/9475A amps of 1964.

Langevin AM16 1964

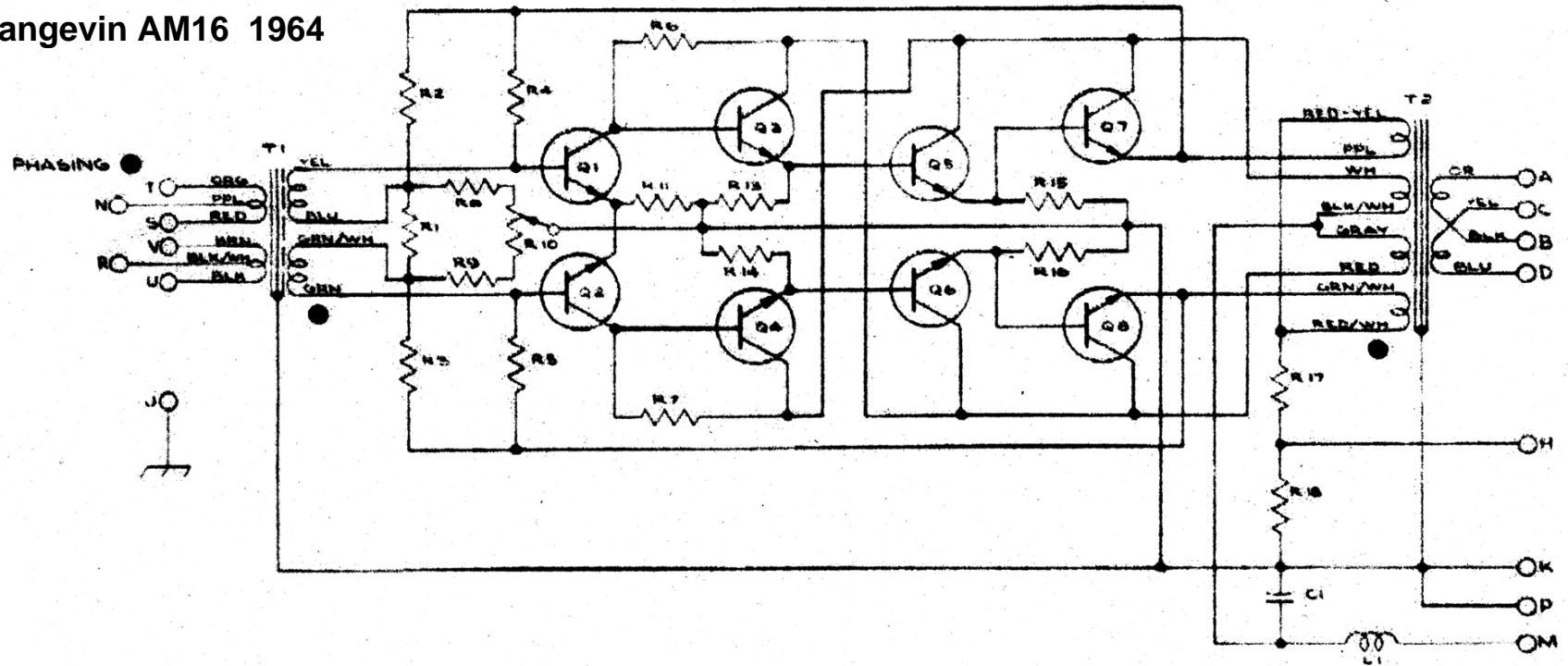

*architects' and engineers' specifications*

The amplifier shall be Langevin AM16. It shall be plug-in. It shall have magnetically and electrostatically shielded input and output transformers. Input impedances shall be 50, 150 and 600 ohms. Output impedances shall be 150 and 600 ohms. All strapping for impedance and "high-low-power" shall be on the tray or cabinet which receives the amplifier, and not on the amplifier proper. Noise level shall not exceed an equivalent input of -127 dbm, un-weighted. Gain at 1 Kc shall be  $45 \pm 0.5$  db. When strapped for high power, harmonic generation at +24 dbm shall not exceed 0.75% from 30 cps to 20 Kc. When on low power, supply current demand shall be reduced, and harmonic generation at +18 dbm shall not exceed 0.5% from 30 cps to 20 Kc. Response at approx. +14 dbm shall be uniform  $\pm 0.5$  db from 20 cps to 20 Kc. Amplifier shall employ only silicon transistors, and no electron tubes. It shall not contain any electrolytic capacitors, nor any part with known shelf or service life. Size shall be approx. 1 3/4" high, 1 1/4" wide, and 10 1/2" long not including plug pins. Plug pins shall be gold-plated. Color scheme shall be gray and iridited cadmium plate.


AM16 AMPLIFIER

# Neve 1073 Channel Amplifier & 1272 Microphone Preamplifier

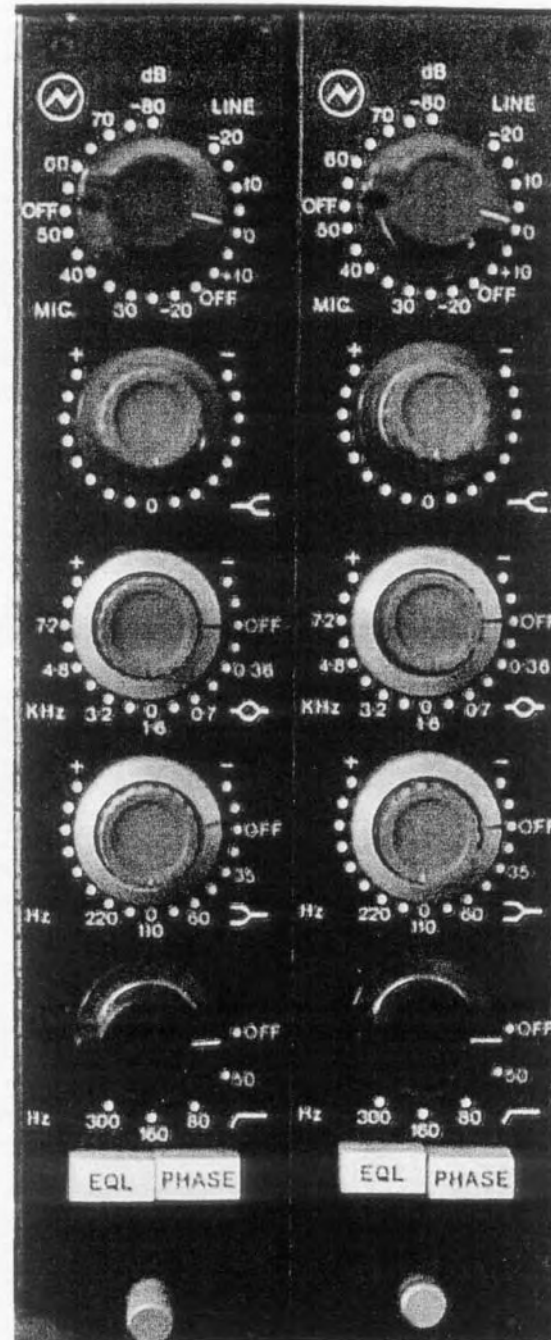
## Manual And Schematics

Including:


- \*Detailed descriptions and schematics for all circuits.
- \*Modifications and parts sources.
- \*Transformer information.



1972

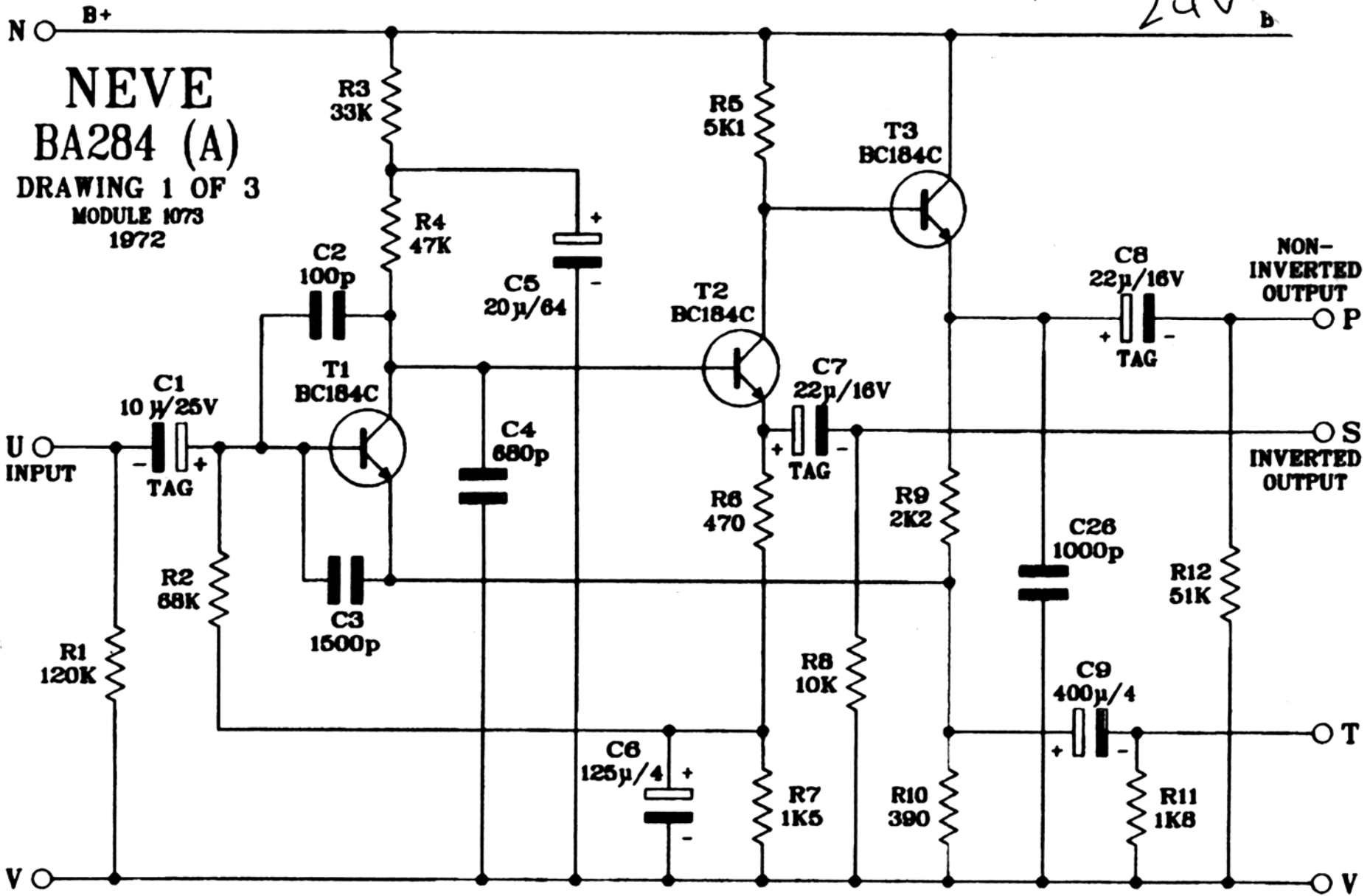



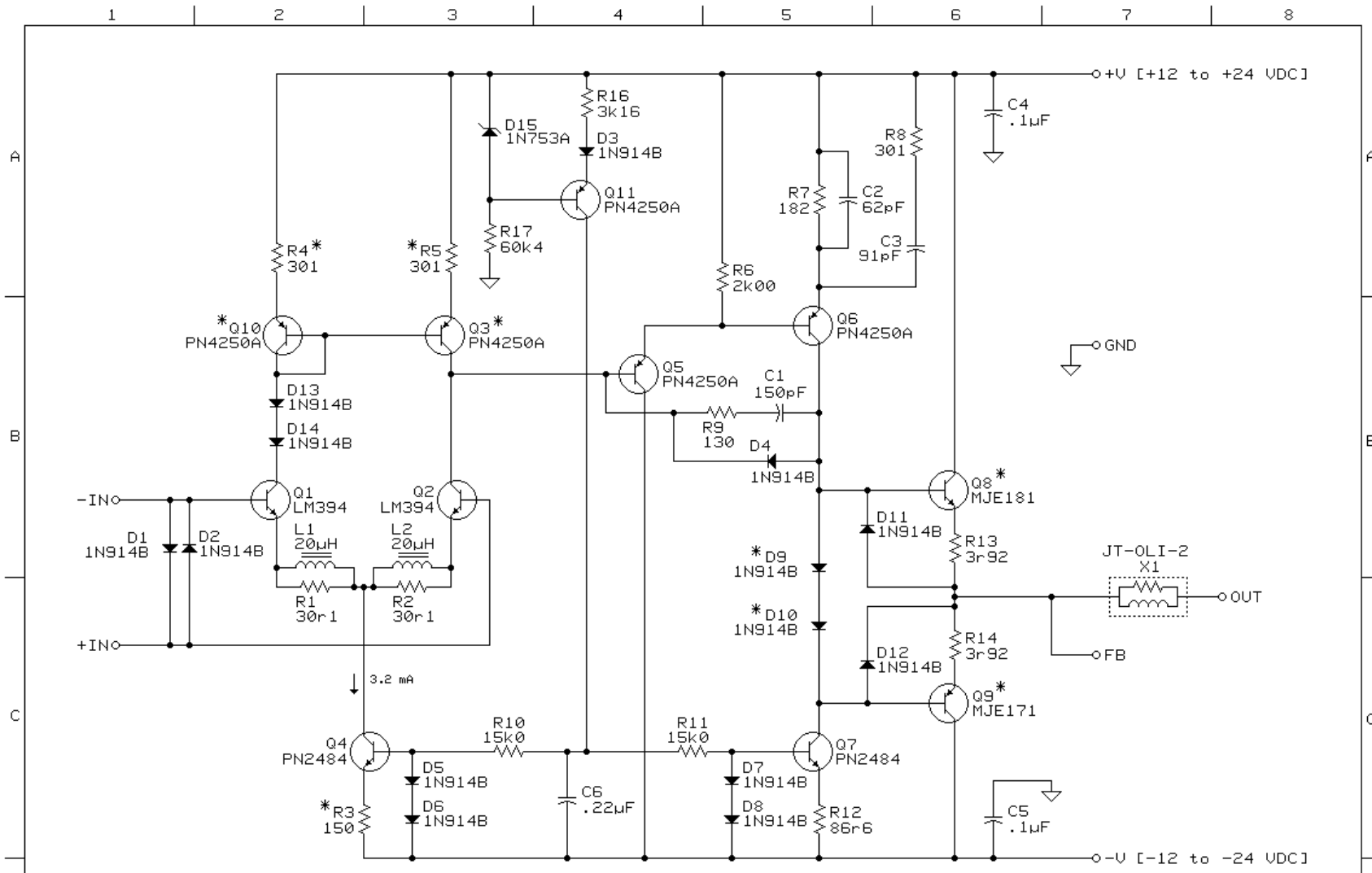


\* INDICATES A PART SELECTED AT TEST, NOMINAL VALUE SHOWN

© COPYRIGHT 1988, JENSEN TRANSFORMERS, INC.  
 THIS CIRCUIT IS COVERED BY U.S. PATENT 4,287,479

		JENSEN TRANSFORMERS, INC. 10735 BURBANK BLVD. N. HOLLYWOOD, CALIFORNIA 91601	
		JT-990-C SCHEMATIC DIAGRAM	
ENGINEER: DEJ/SAH		REVISION: C	
A	SHEET 01 OF 01		JT99-001
	DATE: 02/04/88		
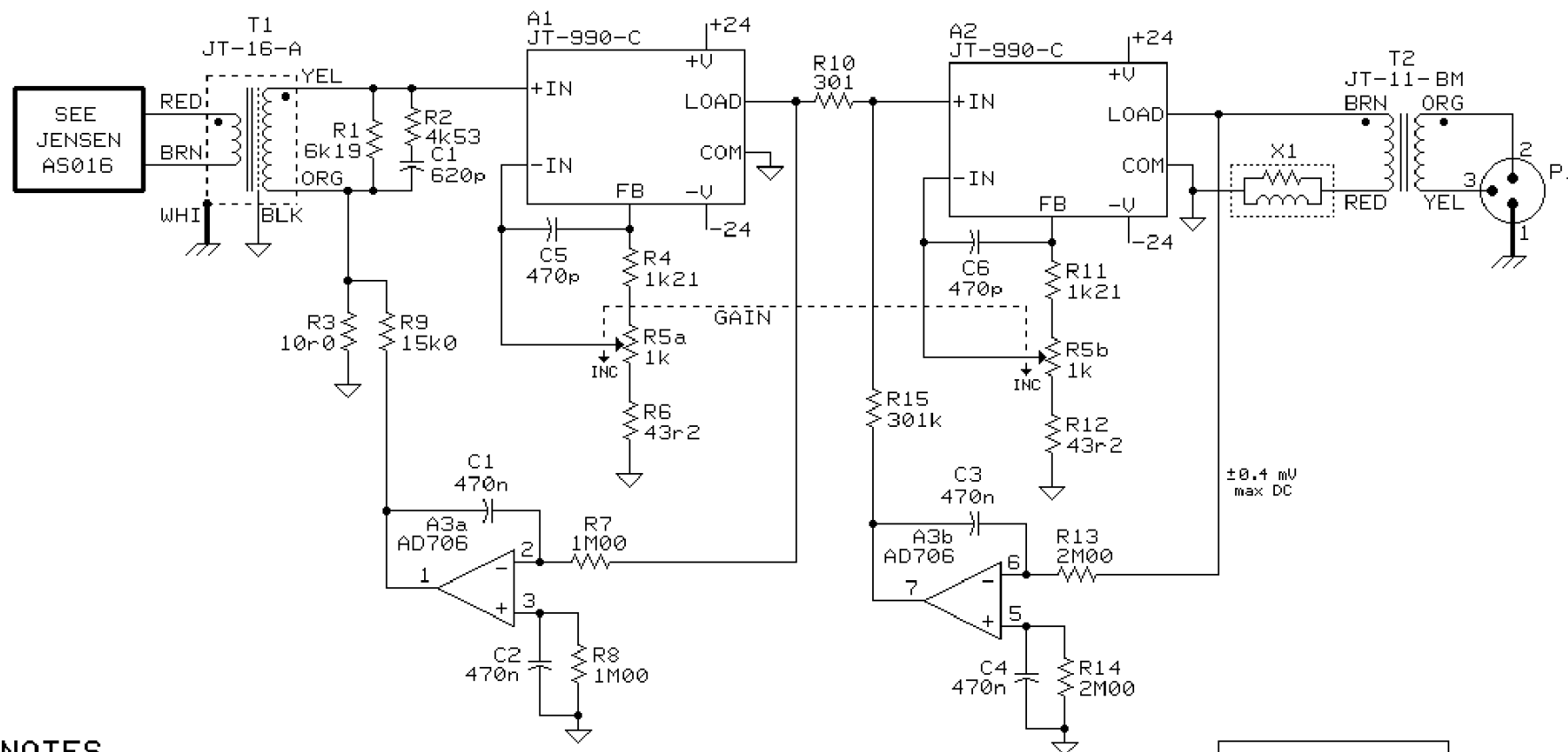
# FAMOUS JENSEN TWIN-SERVO® 990 MIC PREAMP BASIC CIRCUIT



## NOTES

THIS IS NOT A PROJECT FOR ELECTRONIC BEGINNERS ...

THE 990, LIKE ALL HIGH GAIN-BANDWIDTH AMPLIFIERS, CAN OSCILLATE IF CAREFUL ATTENTION IS NOT PAID TO LAYOUT AND GROUNDING. USE OF POWER & GROUND PLANES AND GOOD HIGH FREQUENCY CONSTRUCTION TECHNIQUES IS HIGHLY RECOMMENDED.

R5 IS A REVERSE LOG TAPER CONDUCTIVE PLASTIC DUAL POT

X1 IS AN OUTPUT LOAD ISOLATOR, JENSEN JT-OLI-2 OR EQUIVALENT.

ALL RESISTORS ARE ±1% 1/4w METAL FILM TYPES, ROEDERSTEIN MK2-1 OR EQUIVALENT


ALL CAPACITORS ARE POLYPROPYLENE, POLYSTYRENE, OR NPO/C0G CERAMIC TYPES

43r2 = 43.2 Ω  
 4k53 = 4.53 kΩ  
 2M00 = 2.00 MΩ

<b>jensen</b>	<b>AS083</b>
	03/05/97
7135 HAYVENHURST AVE. VAN NUYS, CALIFORNIA 91406 (818) 374-5857	

# JT-13K6-C IN SIMPLE ONE IC STAGE MIC PREAMP

GAIN VARIABLE FROM 20 dB TO 53 dB

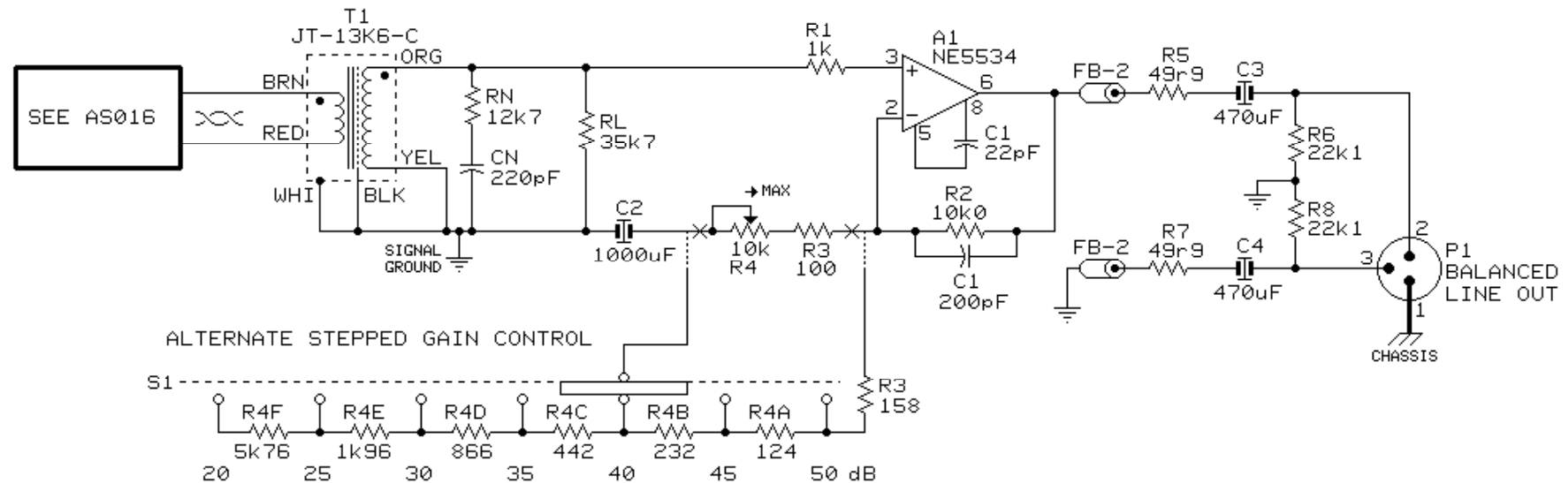

## NOTES

ELECTROLYTIC CAPACITORS ARE PANASONIC BI-POLAR TYPES.

ALL RESISTORS ARE  $\pm 1\%$  1/4w METAL FILM TYPES, ROEDERSTEIN MK2-1 OR EQUIVALENT

ALL RESISTORS IN OHMS ( 12k7 = 12.7k, 49r9 = 49.9 )

POTENTIOMETER R4 IS REVERSE LOG TAPER CONDUCTIVE PLASTIC TYPE

RN, CN, AND RL ARE SPECIFIED ON TRANSFORMER DATA SHEET

MOUNT R1 AS CLOSE AS POSSIBLE TO A1 TO PREVENT POSSIBLE SPURIOUS OSCILLATIONS

USE OF GOLD PLATED CONTACTS IN XLR CONNECTORS IS HIGHLY RECOMMENDED

TIGHTLY TWIST LEADS AS SHOWN  $\infty$  IN PATH FROM J1 TO T1 TO MINIMIZE ELECTROMAGNETIC PICKUP

USE GOOD HIGH FREQUENCY CONSTRUCTION TECHNIQUES AND ADEQUATE POWER SUPPLY BYPASSING AT IC PINS. GROUND PLANE CONSTRUCTION IS HIGHLY RECOMMENDED

S1, IF USED, IS HIGH QUALITY SHORTING TYPE SWITCH



**jensen**

AS017

09/13/95

7135 HAYVENHURST AVE.  
VAN NUYS, CALIFORNIA 91406  
(818) 374-5857



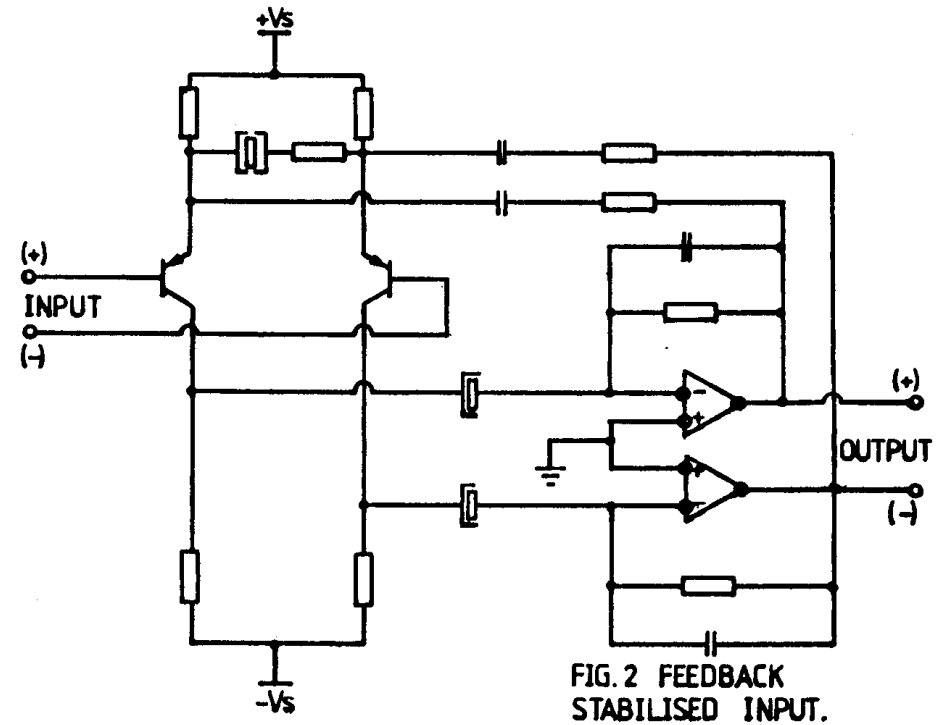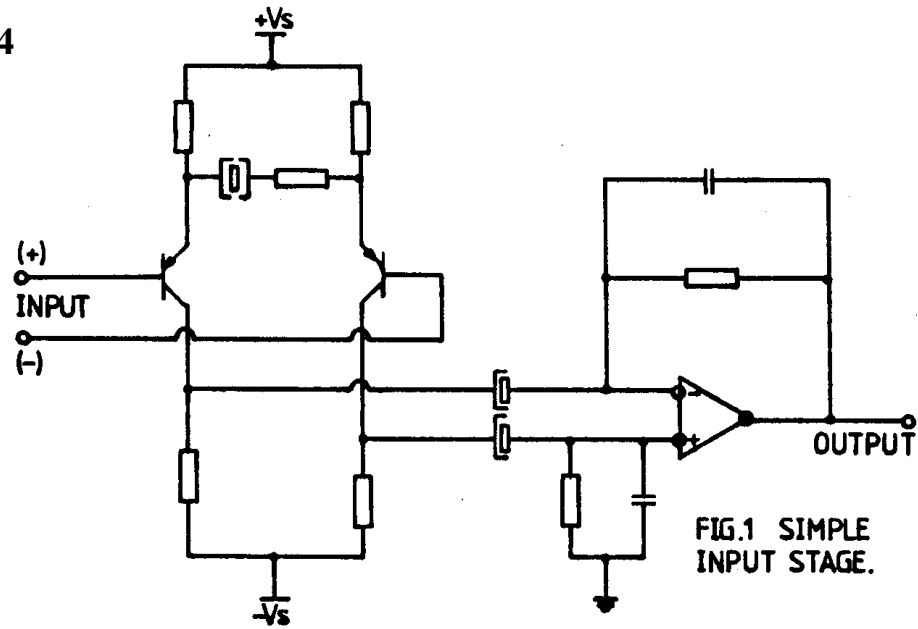

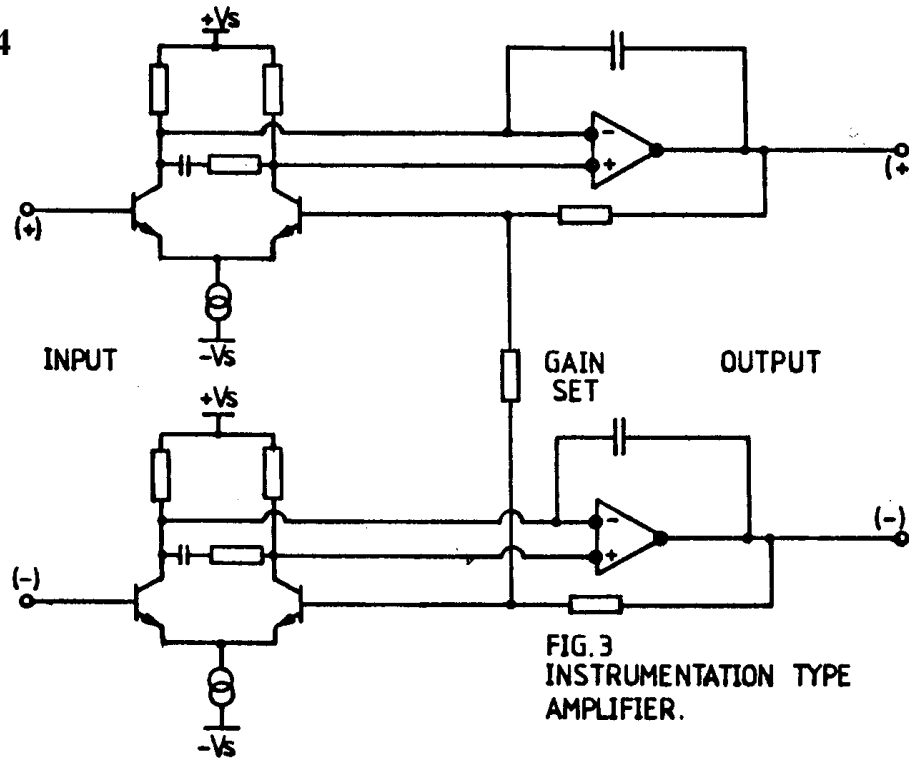


FIG. 3 INSTRUMENTATION TYPE AMPLIFIER.



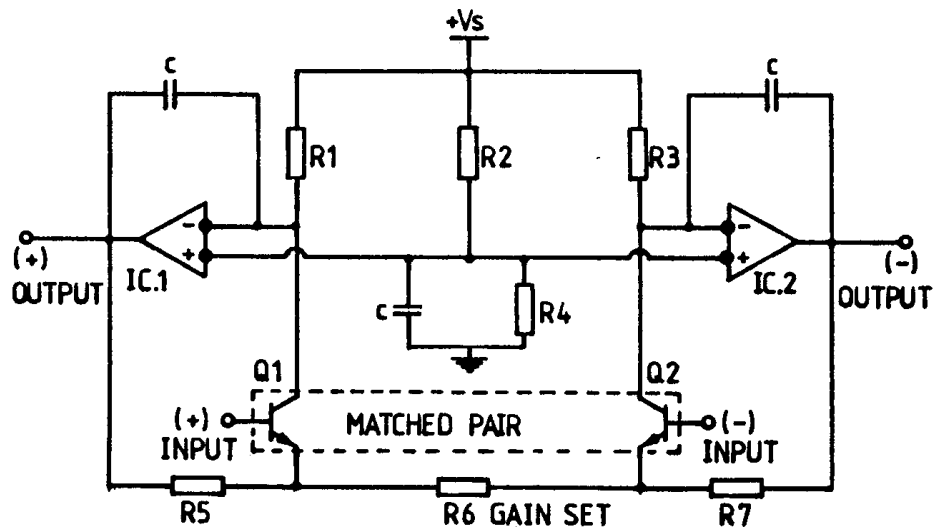
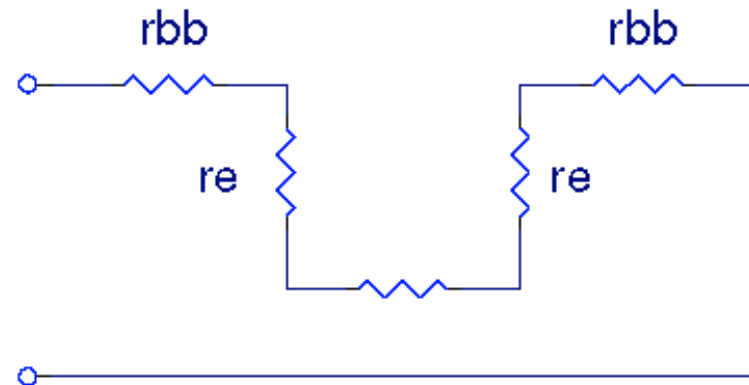


FIG. 4 NEW INPUT STAGE.

Graeme J Cohen.


## Hybrid Input Concept

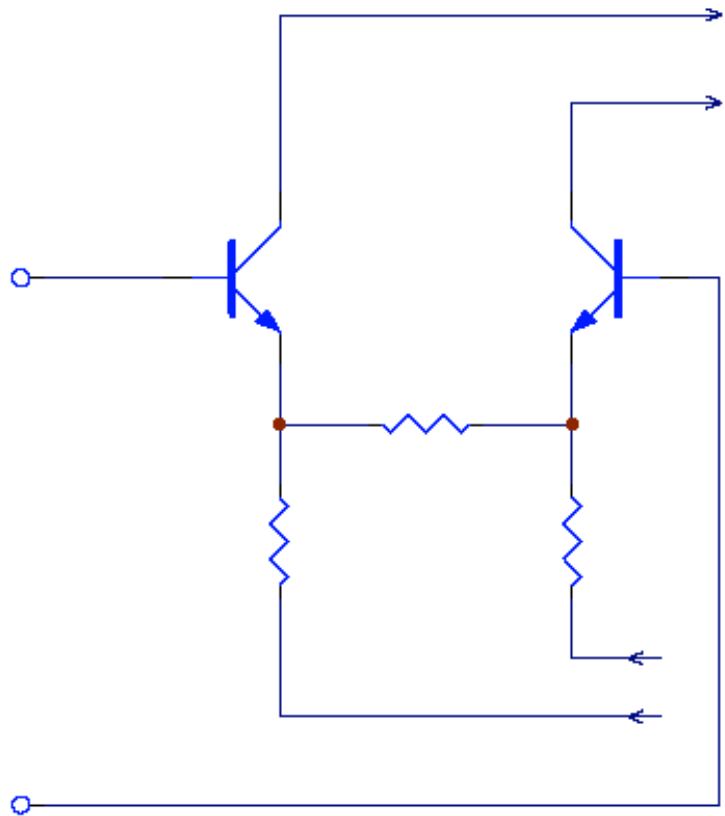


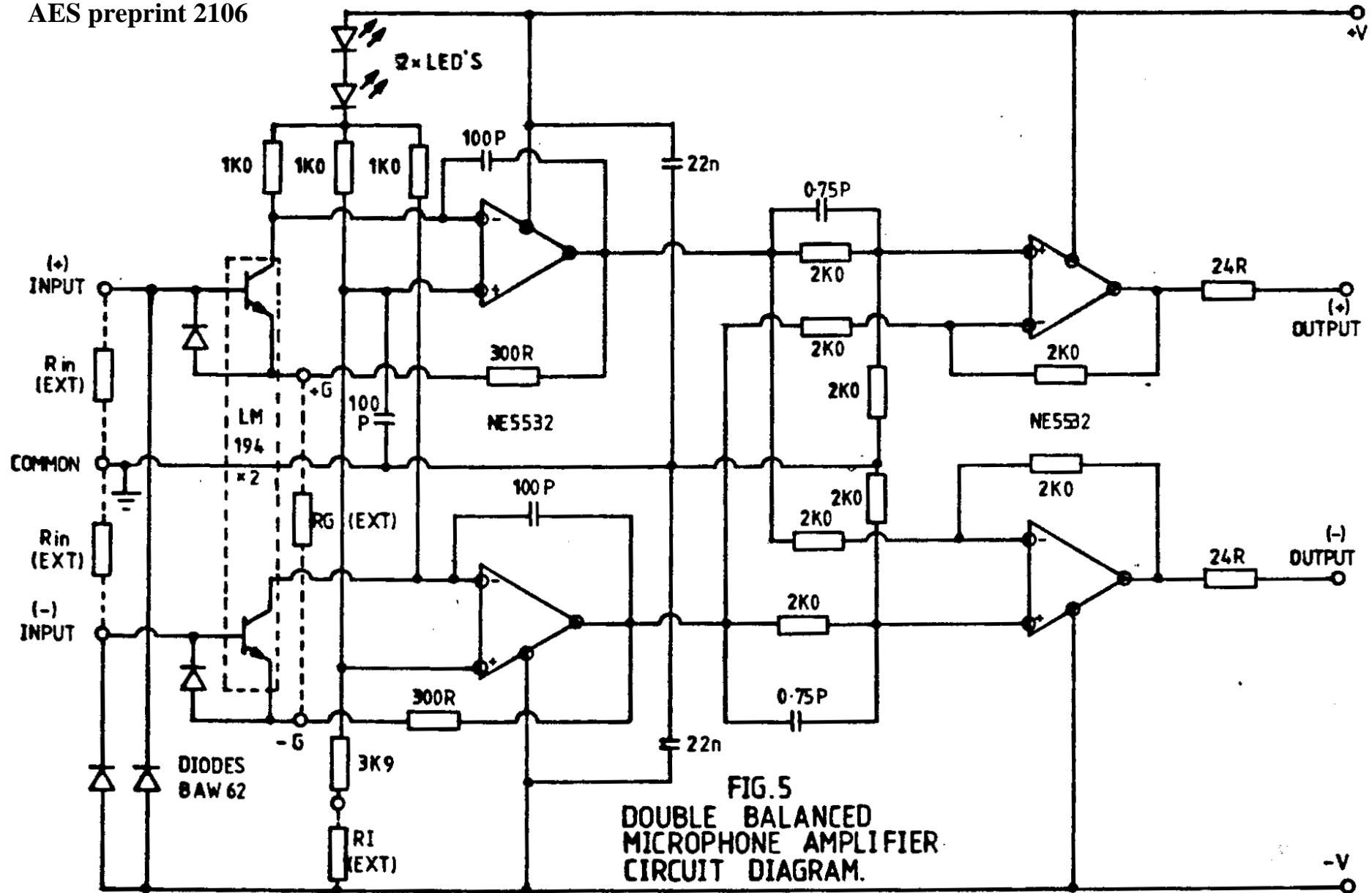

DM 1556

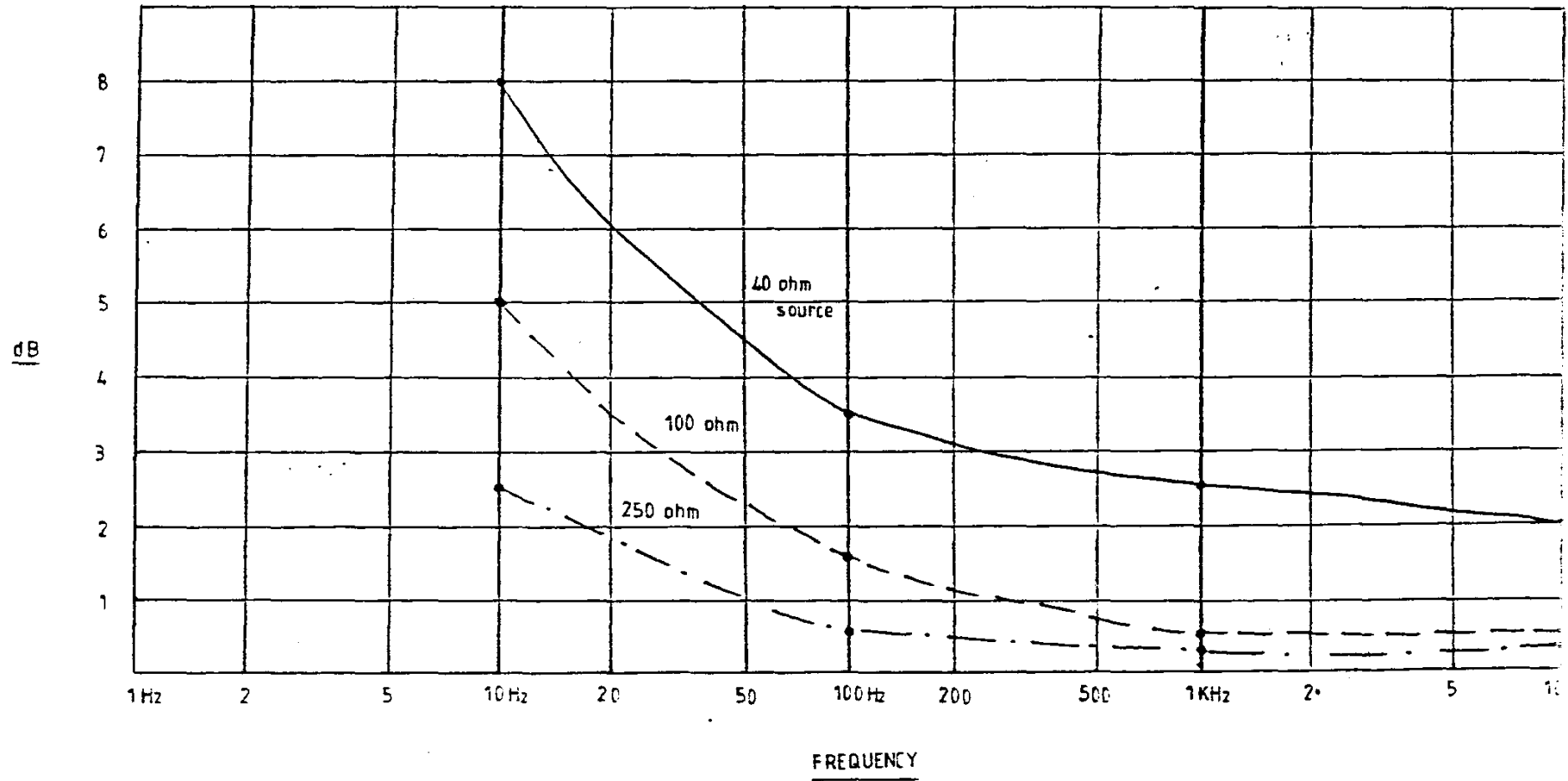TYPICAL NOISE FIGURE FOR  
4mA INPUT STAGE CURRENT



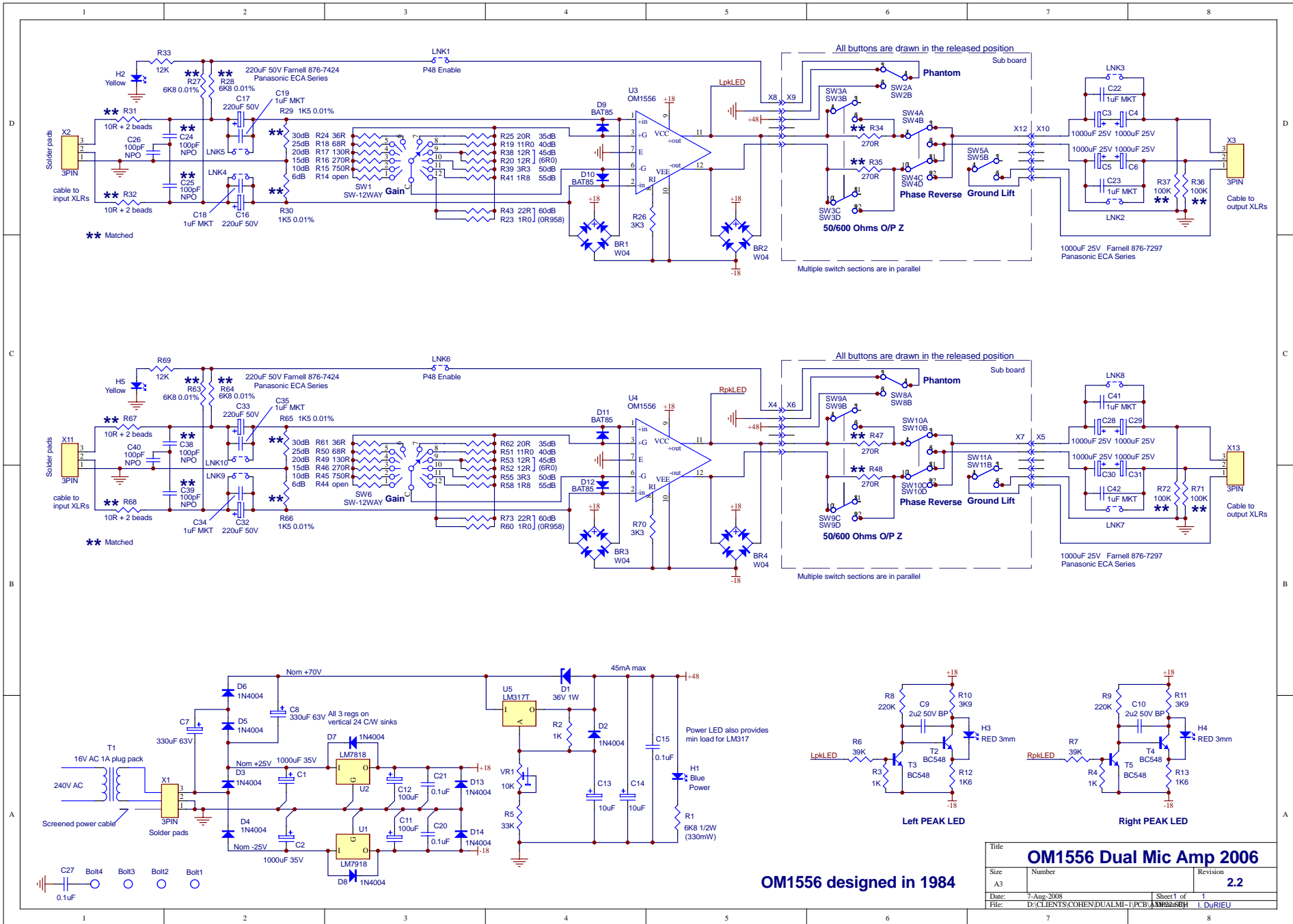

OM1556 designed in 1984

Title			
<b>OM1556 Dual Mic Amp 2006</b>			
Size	Number	Revision	
A3		<b>2.2</b>	
Date:	7-Aug-2008	Sheet 1 of	1
File:	D:\CLIENTS\COHEN\DUALMI-1\PCB\AM1556.SCH	I. DUJRIEU	







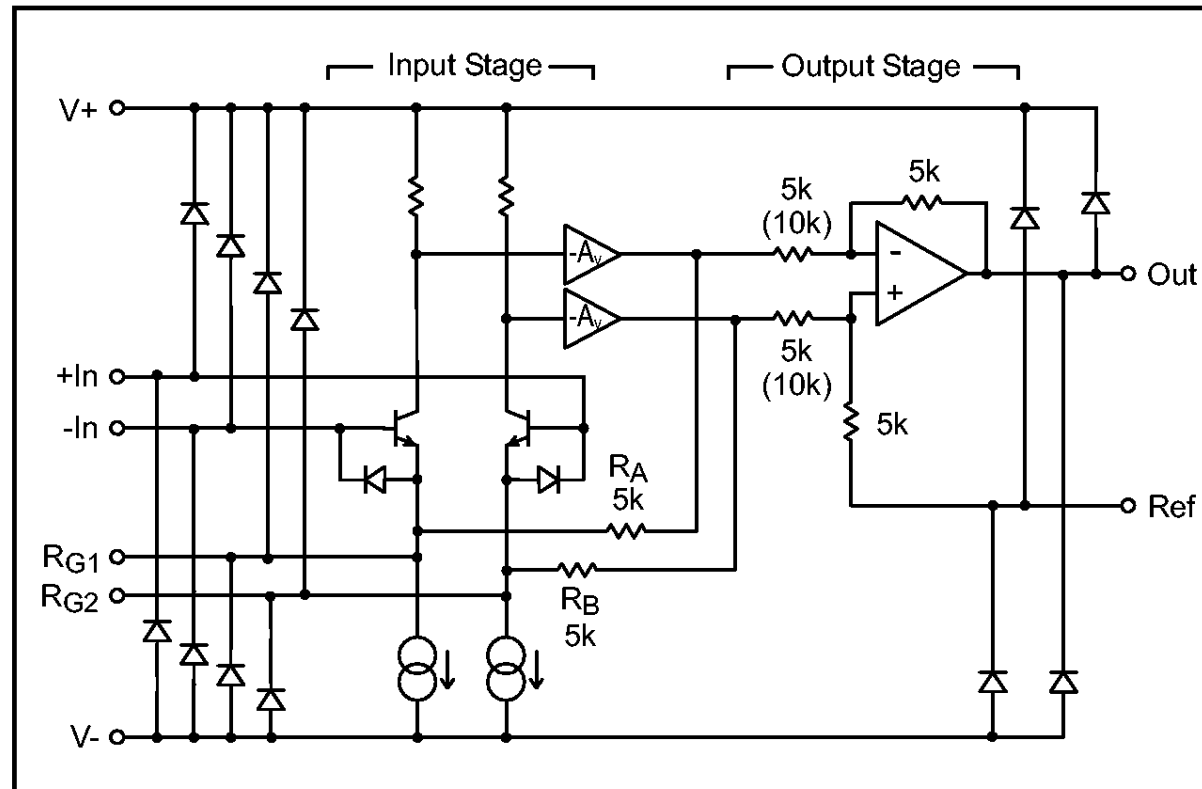


Figure 1. THAT 1510 / 1512 Equivalent Circuit Diagram  
(THAT 1512 values shown in parentheses)

Graeme J Cohen. Sept 1996

# Split Cascode Amplifier

AES preprint 4296

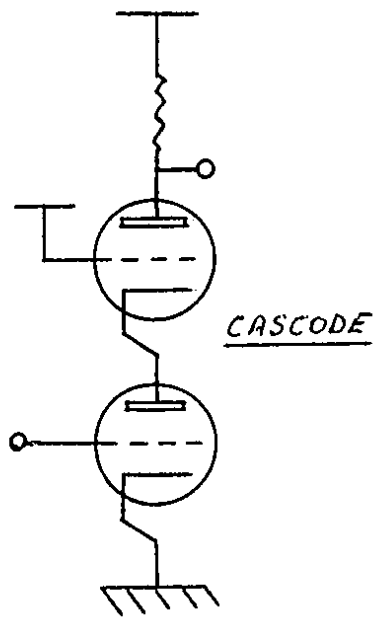


FIG 1

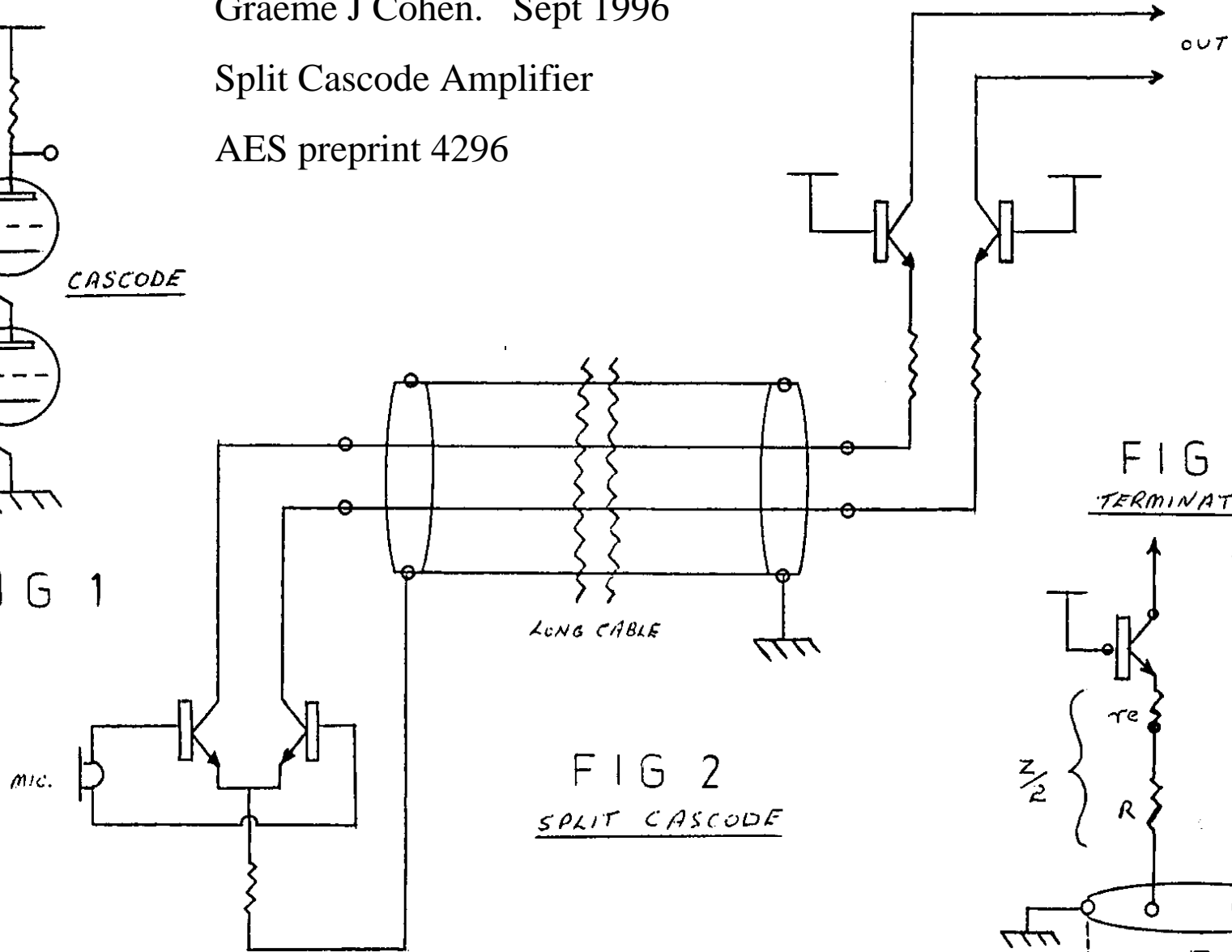


FIG 2  
SPLIT CASCODE

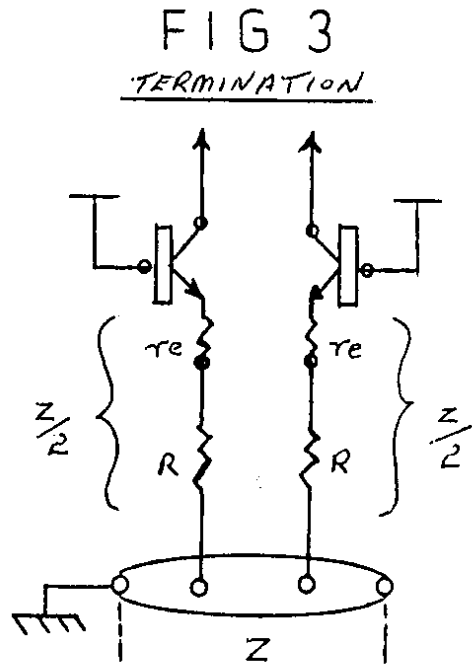


FIG 3


TERMINATION
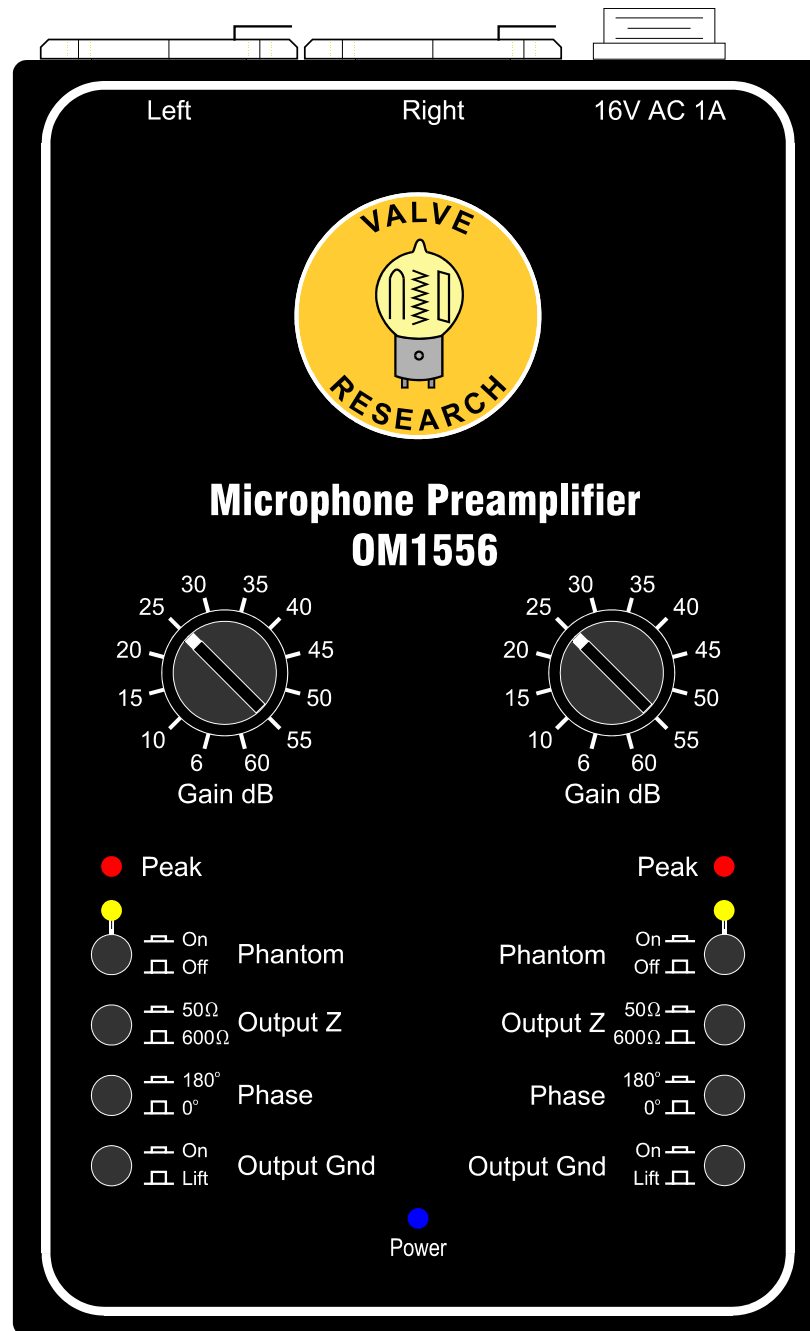
## **TECHNICAL PAPERS (AUDIO)**

- **Double Balanced Microphone Amplifier**  
Presented at the 1984 Australian Regional Convention of the Audio Engineering Society (AES), Melbourne, Australia. Preprint 2106.
- **A Music Amplifier - A New Approach**  
Presented at the 1988 2nd Australian Regional Convention of the AES, Melbourne, Australia. Preprint 2677.
- **A Pulse Test Method for Amplifiers**  
Presented at the 1991 3rd Australian Regional Convention of the AES, Melbourne, Australia. Preprint 3087.
- **A Balanced Analogue Optical Coupler**  
Presented at the 1991 3rd Australian Regional Convention of the AES, Melbourne, Australia. Preprint 3089.
- **Linear Output Stages**  
Presented at the 1993 4th Australian Regional Convention of the AES, Melbourne, Australia. Preprint 3674. Also published in: Glass Audio, Vol. 7, No. 6, 1995.
- **Transmission Line Audio Transformers**  
Presented at the 1993 4th Australian Regional Convention of the AES, Melbourne, Australia. Preprint 3692. Also published in: Glass Audio, Vol. 7, No. 5, 1995.
- **Beam Control Amplifier**  
Presented at the 1995 5th Australian Regional Convention of the AES, Sydney, Australia. Preprint 4026.
- **Dual Single Ended Amplifier**  
Presented at the 1995 5th Australian Regional Convention of the AES, Sydney, Australia. Preprint 4028. Also published in: Glass Audio, Vol. 8, No. 3, 1996.
- **Split Cascade Microphone Amplifier**  
Presented at the 1996 6th Australian Regional Convention of the AES, Melbourne, Australia. Preprint 4296.



Dual OM1556 2006  
OM1556 designed in 1984



Dual OM1556 2006  
 OM1556 designed in 1984