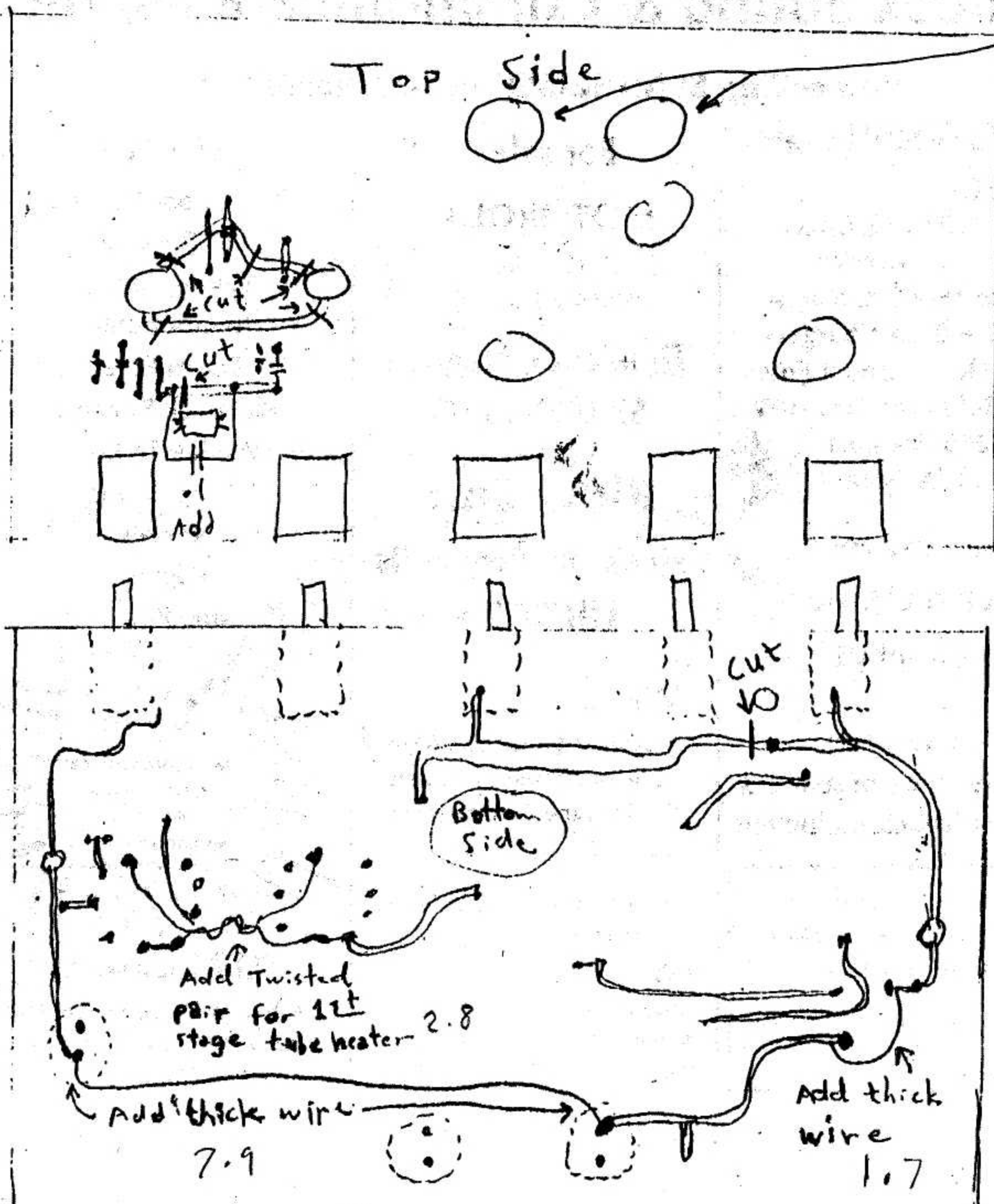


From : Tim Caswell, Studio Electronics 12-19-94

mods to X99 tube circuit board to reduce
hum & noise in clean channel.



optional -
replace filter
caps with
larger values
100 - 150 μF

Add Twisted
pair for 12^t
stage tube heater - 2.8
Add thick wire
7.9

Add thick
wire
1.7