

Whitaker, Jerry C. "Index of Figures"  
*Power Vacuum Tubes Handbook 2<sup>nd</sup> Edition.*  
Ed. Jerry C. Whitaker  
Boca Raton: CRC Press LLC, 2000

# Index of Figures

## Power Vacuum Tube Applications

- Figure 1.1** Patent drawing of a multistage depressed-collector klystron using six collector elements (numbered 16–21). 7
- Figure 1.2** Vacuum tube operating parameters based on power and frequency. 13
- Figure 1.3** Operating frequency bands for shortwave broadcasting. 14
- Figure 1.4** Composite baseband stereo FM signal. A full left-only or right-only signal will modulate the main (L+R) channel to a maximum of 45 percent. The stereophonic subchannel is composed of upper sideband (USB) and lower sideband (LSB) components. 16
- Figure 1.5** Principal elements of a satellite communications link. 19
- Figure 1.6** The power levels in transmission of a video signal via satellite. 20
- Figure 1.7** Simplified block diagram of a pulsed radar system. 21
- Figure 1.8** Direction-finding error resulting from beacon reflections. 25
- Figure 1.9** The concept of two-way distance ranging. 26
- Figure 1.10** The concept of differential distance ranging (hyperbolic). 27
- Figure 1.11** The concept of one-way distance ranging. 27
- Figure 1.12** Basic schematic of a 20 kW induction heater circuit. 30
- Figure 1.13** The electromagnetic spectrum. 31

## Modulation Systems and Characteristics

- Figure 2.1** Characteristics of a series resonant circuit as a function of frequency for a constant applied voltage and different circuit  $Q$ s: (a) magnitude, (b) phase angle. 40
- Figure 2.2** Characteristics of a parallel resonant circuit as a function of frequency for different circuit  $Q$ s: (a) magnitude, (b) phase angle. 41
- Figure 2.3** Cylindrical resonator incorporating a coupling loop: (a) orientation of loop with respect to cavity, (b) equivalent coupled circuit. 44
- Figure 2.4** Cross section of a quartz crystal taken in the plane perpendicular to the optical axis: (a)  $Y$ -cut plate, (b)  $X$ -cut plate. 44
- Figure 2.5** The effects of temperature on two types of AT-cut crystals. 45
- Figure 2.6** Equivalent network of a piezoelectric resonator. 46
- Figure 2.7** Frequency vs. temperature characteristics for a typical temperature-compensated crystal oscillator. 48
- Figure 2.8** Plate efficiency as a function of conduction angle for an amplifier with a tuned load. 51
- Figure 2.9** A plot of signal power vs. frequency for white noise and frequency limited noise. 54
- Figure 2.10** Frequency-domain representation of an amplitude-modulated signal at 100 percent modulation.  $E_c$  = carrier power,  $F_c$  = frequency of the carrier, and  $F_m$  = frequency of the modulating signal. 56

- Figure 2.11** Time-domain representation of an amplitude-modulated signal. Modulation at 100 percent is defined as the point at which the peak of the waveform reaches twice the carrier level, and the minimum point of the waveform is zero. 57
- Figure 2.12** Simplified diagram of a high-level amplitude-modulated amplifier. 59
- Figure 2.13** Idealized amplitude characteristics of the FCC standard waveform for monochrome and color TV transmission. 60
- Figure 2.14** Types of suppressed carrier amplitude modulation: (a) the modulating signal, (b) double-sideband AM signal, (c) double-sideband suppressed carrier AM, (d) single-sideband suppressed carrier AM. 61
- Figure 2.15** Simplified QAM modulator. 62
- Figure 2.16** Simplified QAM demodulator. 63
- Figure 2.17** Plot of Bessel functions of the first kind as a function of modulation index. 65
- Figure 2.18** RF spectrum of a frequency-modulated signal with a modulation index of 5 and other operating parameters as shown. 67
- Figure 2.19** RF spectrum of a frequency-modulated signal with a modulation index of 15 and operating parameters as shown. 67
- Figure 2.20** Preemphasis curves for time constants of 50, 75, and 100  $\mu\text{s}$ . 69
- Figure 2.21** Block diagram of an FM exciter. 70
- Figure 2.22** Simplified reactance modulator. 71
- Figure 2.23** Equivalent circuit of the reactance modulator. 72
- Figure 2.24** Vector diagram of a reactance modulator producing FM. Note:  $V_g = V_{c2}$ . 72
- Figure 2.25** Voltage-controlled direct-FM modulator. 72
- Figure 2.26** Mechanical layout of a common type of  $\frac{1}{4}$ -wave PA cavity for FM service. 73
- Figure 2.27** Pulse amplitude modulation waveforms: (a) modulating signal; (b) square-topped sampling, bipolar pulse train; (c) topped sampling, bipolar pulse train; (d) square-topped sampling, unipolar pulse train; (e) top sampling, unipolar pulse train. 76
- Figure 2.28** Pulse time modulation waveforms: (a) modulating signal and sample-and-hold (S/H) waveforms, (b) sawtooth waveform added to S/H, (c) leading-edge PTM, (d) trailing-edge PTM. 77
- Figure 2.29** Pulse frequency modulation. 78
- Figure 2.30** The quantization process. 78
- Figure 2.31** Delta modulation waveforms: (a) modulating signal, (b) quantized modulating signal, (c) pulse train, (d) resulting delta modulation waveform. 80
- Figure 2.32** Binary FSK waveform. 81
- Figure 2.33** Binary PSK waveform. 81
- Figure 2.34** Various baseband modulation formats: (a) non-return-to zero, (b) unipolar-return-to-zero, (c) differential encoded (NRZ-mark), (d) split phase. 83

#### Vacuum Tube Principles

- Figure 3.1** Variation of electron emission as a function of absolute temperature for a thoriated-tungsten emitter. 91
- Figure 3.2** Common types of heater and cathode structures. 91
- Figure 3.3** Ratio of secondary emission current to primary current as a function of primary electron velocity. 92

- Figure 3.4** Vacuum diode: (a) directly heated cathode, (b) indirectly heated cathode. 93
- Figure 3.5** Anode current as a function of anode voltage in a two-electrode tube for three cathode temperatures. 93
- Figure 3.6** Mechanical configuration of a power triode. 95
- Figure 3.7** Constant-current characteristics for a triode with a  $\mu$  of 12. 97
- Figure 3.8** Constant-current characteristics for a triode with a  $\mu$  of 20. 98
- Figure 3.9** Grounded-grid constant-current characteristics for a zero-bias triode with a  $\mu$  of 200. 98
- Figure 3.10** Internal configuration of a planar triode. 99
- Figure 3.11** Tetrode plate current characteristics. Plate current is plotted as a function of plate voltage, with grid voltages as shown. 100
- Figure 3.12** Radial beam power tetrode (4CX15000A). 101
- Figure 3.13** Principal dimensions of 4CX15000A tetrode. 103
- Figure 3.14** 5CX1500B power pentode device. 105
- Figure 3.15** Principal dimensions of 5CX1500B pentode. 108
- Figure 3.16** Continuous wave output power capability of a gridded vacuum tube. 109
- Figure 3.17** Performance of a class C amplifier as the operating frequency is increased beyond the design limits of the vacuum tube. 109
- Figure 3.18** Transit-time effects in a class C amplifier: (a) control grid voltage, (b) electron position as a function of time (triode case), (c) electron position as a function of time (tetrode case), (d) plate current (triode case). 111
- Figure 3.19** The relationship between anode dissipation and cooling method. 113
- Figure 3.20** A typical transmitter PA stage cooling system. 113
- Figure 3.21** Water-cooled anode with grooves for controlled water flow. 114
- Figure 3.22** Typical vapor-phase cooling system. 115
- Figure 3.23** Vapor-phase cooling system for a 4-tube transmitter using a common water supply. 116
- Figure 3.24** Photo of a typical oxide cathode. 118
- Figure 3.25** Spiral-type tungsten filament. 120
- Figure 3.26** Bar-type tungsten filament. 120
- Figure 3.27** Mesh tungsten filament. 121
- Figure 3.28** Mesh grid structure. 122
- Figure 3.29** Pyrolytic graphite grid: (a) before laser processing, (b) completed assembly. 124
- Figure 3.30** The screen grid assembly of a typical tetrode PA tube. 125
- Figure 3.31** The internal arrangement of the anode, screen, control grid, and cathode assemblies of a tetrode power tube. 125
- Figure 3.32** Circuit for providing a low-impedance screen supply for a tetrode. 126
- Figure 3.33** Series power supply configuration for swamping the screen circuit of a tetrode. 127
- Figure 3.34** Typical curve of grid current as a function of control grid voltage for a high-power thoriated-tungsten filament tetrode. 128
- Figure 3.35** Secondary emission characteristics of various metals under ordinary conditions. 128
- Figure 3.36** A cutaway view of the anode structure of an RF power amplifier tube. 130
- Figure 3.37** Thermal conductivity of common ceramics. 131

- Figure 3.38** Cross section of the base of a tetrode socket showing the connection points. 134
- Figure 3.39** The elements involved in the neutralization of a tetrode PA stage. 135
- Figure 3.40** A graphical representation of the elements involved in the self-neutralization of a tetrode RF stage. 136
- Figure 3.41** Push-pull grid neutralization. 137
- Figure 3.42** Symmetrical stage neutralization for a grounded-grid circuit. 138
- Figure 3.43** Push-pull grid neutralization in a single-ended tetrode stage. 138
- Figure 3.44** Single-ended grid neutralization for a tetrode. 139
- Figure 3.45** The previous figure redrawn to show the elements involved in neutralization. 139
- Figure 3.46** Single-ended plate neutralization. 140
- Figure 3.47** Single-ended plate neutralization showing the capacitance bridge present. 140
- Figure 3.48** A grounded-screen PA stage neutralized through the use of stray inductance between the screen connector and the cavity deck: (a) schematic diagram, (b) mechanical layout of cavity. 142
- Figure 3.49** Circuit of grounded-grid amplifier having grid impedance and neutralized for reactive currents. 143
- Figure 3.50** Neutralization by cross-connected capacitors of a symmetrical cathode-excited amplifier with compensation of lead inductance. 144
- Figure 3.51** Graphical representation of the elements of a tetrode when self-neutralized. 145
- Figure 3.52** Components of the output voltage of a tetrode when neutralized by adding series screen-lead capacitance. 146
- Figure 3.53** Components of the output voltage of a tetrode when neutralized by adding external grid-to-plate capacitance. 146
- Figure 3.54** Components of the output voltage of a tetrode neutralized by adding inductance common to the screen and cathode return. 147

#### Designing Vacuum Tube Circuits

- Figure 4.1** Plate efficiency as a function of conduction angle for an amplifier with a tuned load. 152
- Figure 4.2** Basic grounded-cathode RF amplifier circuit. 153
- Figure 4.3** Typical amplifier circuit using a zero-bias triode. Grid current is measured in the return lead from ground to the filament. 154
- Figure 4.4** Variation of plate voltage as a function of grid voltage. 155
- Figure 4.5** Relationship between grid voltage and plate voltage plotted on a constant-current curve. 155
- Figure 4.6** Instantaneous values of plate and grid current as a function of time. 156
- Figure 4.7** Schematic of a tetrode RF power amplifier showing tube element bypass capacitors. 162
- Figure 4.8** Schematic of a triode RF power amplifier showing tube element bypass capacitors: (a) control grid at dc ground potential, (b) control grid bypassed to ground. 163
- Figure 4.9** Interelectrode capacitances supporting VHF parasitic oscillation in a high-frequency RF amplifier. 164

- Figure 4.10** Placement of parasitic suppressors to eliminate VHF parasitic oscillations in a high-frequency RF amplifier: (a) resistor-coil combination, (b) parasitic choke. 165
- Figure 4.11** A section of honeycomb shielding material used in an RF amplifier. 168
- Figure 4.12** A selection of common fingerstock. 169
- Figure 4.13** Shorted  $\frac{1}{4}$ -wavelength line: (a) physical circuit, (b) electrical equivalent. 172
- Figure 4.14** Shorted line less than  $\frac{1}{4}$  wavelength: (a) physical circuit, (b) electrical equivalent. 172
- Figure 4.15** A simplified representation of the grid input circuit of a PA tube. 174
- Figure 4.16** Three common methods for RF bypassing of the cathode of a tetrode PA tube: (a) grounding the cathode below 30 MHz, (b) grounding the cathode above 30 MHz, (c) grounding the cathode via a  $\frac{1}{2}$ -wave transmission line. 175
- Figure 4.17** RF circulating current path between the plate and screen in a tetrode PA tube. 176
- Figure 4.18** The physical layout of a common type of  $\frac{1}{4}$ -wavelength PA cavity designed for VHF operation. 177
- Figure 4.19** The RF circulating current paths for the  $\frac{1}{4}$ -wavelength cavity shown in Figure 4.18. 178
- Figure 4.20** Graph of the RF current, RF voltage, and RF impedance for a  $\frac{1}{4}$ -wavelength shorted transmission line. At the feed point, RF current is zero, RF voltage is maximum, and RF impedance is infinite. 178
- Figure 4.21** Graph of the RF current, RF voltage, and RF impedance produced by the physically foreshortened coaxial transmission line cavity. 179
- Figure 4.22** Basic loading mechanism for a VHF  $\frac{1}{4}$ -wave cavity. 180
- Figure 4.23** The  $\frac{1}{2}$ -wavelength PA cavity in its basic form. 181
- Figure 4.24** The distribution of RF current, voltage, and impedance along the inner conductor of a  $\frac{1}{2}$ -wavelength cavity. 182
- Figure 4.25** The configuration of a practical  $\frac{1}{2}$ -wavelength PA cavity. 183
- Figure 4.26** Coarse-tuning mechanisms for a  $\frac{1}{2}$ -wave cavity. 184
- Figure 4.27** Using the cavity's movable section to adjust for resonance: (a) the rotary section at maximum height, (b) the rotary section at minimum height. 185
- Figure 4.28** The basic design of a folded  $\frac{1}{2}$ -wavelength cavity. 186
- Figure 4.29** Double-tuned overcoupled broadband cavity amplifier. 188
- Figure 4.30** The use of inductive coupling in a  $\frac{1}{4}$ -wavelength PA stage. 189
- Figure 4.31** Top view of a cavity showing the inductive coupling loop rotated away from the axis of the magnetic field of the cavity. 189
- Figure 4.32** Cutaway view of the cavity showing the coupling loop rotated away from the axis of the magnetic field. 190
- Figure 4.33** A  $\frac{1}{4}$ -wavelength cavity with capacitive coupling to the output load. 191
- Figure 4.34** The equivalent circuit of a  $\frac{1}{4}$ -wavelength cavity amplifier with capacitive coupling. 192
- Figure 4.35** The equivalent circuit of a  $\frac{1}{4}$ -wavelength cavity amplifier showing how series capacitive coupling appears electrically as a parallel circuit to the PA tube. 192
- Figure 4.36** Typical VHF cavity amplifier. 194
- Figure 4.37** Electrical equivalent of the cavity amplifier shown in Figure 4.36. 195

- Figure 4.38** VHF cavity amplifiers: (a, above) cross-sectional view of a broadband design, (b, below) cavity designed for television service, (c, next page) FM broadcast cavity amplifier. 196
- Figure 4.39** Conventional capacitor input filter full-wave bridge. 198
- Figure 4.40** A portion of a high-voltage series-connected rectifier stack. 199
- Figure 4.41** A 3-phase delta-connected high-voltage rectifier. 199
- Figure 4.42** High-voltage rectifier assembly for a 3-phase delta-connected circuit. 200
- Figure 4.43** Using buildout resistances to force current sharing in a parallel rectifier assembly. 201
- Figure 4.44** Inverse-parallel thyristor ac power control: (a) circuit diagram, (b) voltage and current waveforms for full and reduced thyristor control angles. The waveforms apply for a purely resistive load. 202
- Figure 4.45** Waveforms in an ac circuit using thyristor power control. 203
- Figure 4.46** Voltage and current waveforms for inverse-parallel thyristor power control with an inductive load: (a) full conduction, (b) small-angle phase reduction, (c) large-angle phase reduction. 204
- Figure 4.47** Modified full-thyristor 3-phase ac control of an inductive delta load. 205
- Figure 4.48** A 6-phase boost rectifier circuit. 206
- Figure 4.49** Thyristor-controlled high-voltage servo power supply. 207
- Figure 4.50** Phase-controlled power supply with primary regulation. 208
- Figure 4.51** Simplified block diagram of the gating circuit for a phase-control system using back-to-back SCRs. 209
- Figure 4.52** Basic 3-phase rectifier circuits: (a) half-wave wye, (b) full-wave bridge, (c) 6-phase star, (d) 3-phase double-wye. 211
- Figure 4.53** Voltage and current waveshapes for an inductive-input filter driven by a 3-phase supply. 214
- Figure 4.54** Characteristics of a capacitive input filter circuit: (a) schematic diagram, (b) voltage waveshape across the input capacitor, (c) waveshape of current flowing through the diodes. 217
- Figure 4.55** Plate voltage sampling circuits: (a) single-ended, (b) differential. 218
- Figure 4.56** Differential amplifier circuits: (a) basic circuit, (b) instrumentation amplifier. 219
- Figure 4.57** Transmitter high-voltage power supply showing remote plate current and voltage sensing circuits. 220

#### Applying Vacuum Tube Devices

- Figure 5.1** The classic plate-modulated PA circuit for AM applications. 224
- Figure 5.2** Basic methods of screen and plate modulation: (a) plate modulation, (b) plate and screen modulation, (c) plate modulation using separate plate/screen supplies. 225
- Figure 5.3** Grid modulation of a class C RF amplifier. 226
- Figure 5.4** Cathode modulation of a class C RF amplifier. 227
- Figure 5.5** Classic vacuum tube class C amplifier: (a) representative waveforms, (b) schematic diagram. Conditions are as follows: sinusoidal grid drive, 120° anode current, resonant anode load. 228
- Figure 5.6** Class B push-pull modulator stage for a high-level AM amplifier. 229
- Figure 5.7** The pulse duration modulation (PDM) method of pulse width modulation. 230

- Figure 5.8** The principal waveforms of the PDM system. 231
- Figure 5.9** Block diagram of a PDM waveform generator. 232
- Figure 5.10** Spectrum at the output of a nonlinear device with an input of two equal-amplitude sine waves of  $f_1 = 2.001$  MHz and  $f_2 = 2.003$  MHz. 235
- Figure 5.11** Ideal grid-plate transfer curve for class AB operation. 236
- Figure 5.12** Simplified schematic diagram of the Chireix outphasing modulated amplifier: (a) output circuit, (b) drive signal generation circuit. 238
- Figure 5.13** Doherty high-efficiency AM amplifier: (a) operating theory, (b) schematic diagram of a typical system. 239
- Figure 5.14** Screen-modulated Doherty-type circuit. 241
- Figure 5.15** Practical implementation of a screen-modulated Doherty-type 1 MW power amplifier (Continental Electronics). 242
- Figure 5.16** Terman-Woodyard high-efficiency modulated amplifier. 243
- Figure 5.17** Dome high-efficiency modulated amplifier. 244
- Figure 5.18** Basic block diagram of a TV transmitter. The three major subassemblies are the exciter, IPA, and PA. The power supply provides operating voltages to all sections, and high voltage to the PA stage. 247
- Figure 5.19** Schematic diagram of a 60 kW klystron-based TV transmitter. 249
- Figure 5.20** Schematic diagram of the modulator section of a 60 kW TV transmitter. 250
- Figure 5.21** Cathode-driven triode power amplifier. 251
- Figure 5.22** Grid-driven grounded-screen tetrode power amplifier. 254
- Figure 5.23** Input matching circuits: (a) inductive input matching, (b) capacitive input matching. 256
- Figure 5.24** Interstage RF coupling circuits: (a) variable capacitance matching, (b) variable tank matching, (c) variable pi matching, (d) fixed broadband impedance-transformation network. 257
- Figure 5.25** Two common approaches to automatic frequency control of a magnetron oscillator. 259
- Figure 5.26** Digital synchronizer system for radar applications. 260
- Figure 5.27** A line-type modulator for radar. 261
- Figure 5.28** Active-switch modulator circuits: (a) direct-coupled system, (b) capacitor-coupled, (c) transformer-coupled, (d) capacitor- and transformer-coupled. 262
- Figure 5.29** A magnetic modulator circuit. 262

#### Microwave Power Tubes

- Figure 6.1** Microwave power tube type as a function of frequency and output power. 267
- Figure 6.2** Types of linear-beam microwave tubes. 268
- Figure 6.3** Schematic diagram of a linear-beam tube. 268
- Figure 6.4** Types of crossed-field microwave tubes. 269
- Figure 6.5** Magnetron electron path looking down into the cavity with the magnetic field applied. 269
- Figure 6.6** Family tree of the distributed emission crossed-field amplifier (CFA). 270
- Figure 6.7** Cross section of a 7289 planar triode. 272
- Figure 6.8** Grounded-grid equivalent circuits: (a) low-frequency operation, (b) microwave-frequency operation. The cathode-heating and grid-bias circuits are not shown. 273



- Figure 6.9** Cutaway view of the tetrode (*left*) and the Diacrode (*right*). Note that the RF current peaks above and below the Diacrode center while on the tetrode there is only one peak at the bottom. 274
- Figure 6.10** The elements of the Diacrode, including the upper cavity. Double current, and consequently double power, is achieved with the device because of the current peaks at the top and bottom of the tube, as shown. 275
- Figure 6.11** Schematic representation of a reflex klystron. 276
- Figure 6.12** Position-time curves of electrons in the anode-repeller space, showing the tendency of the electrons to bunch around the electron passing through the anode at the time when the alternating gap voltage is zero and becoming negative. 277
- Figure 6.13** Schematic cross section of a reflex klystron oscillator. 279
- Figure 6.14** Cross section of a classic two-cavity klystron oscillator. 280
- Figure 6.15** Principal elements of a klystron. 282
- Figure 6.16** Klystron cavity: (*a*) physical arrangement, (*b*) equivalent circuit. 283
- Figure 6.17** Bunching effect of a multicavity klystron. 284
- Figure 6.18** Diode section of a klystron electron gun. 285
- Figure 6.19** Beam forming in the diode section of a klystron electron gun. 285
- Figure 6.20** Klystron beam-current variation as a function of emitter temperature. 286
- Figure 6.21** Modulating-anode electrode in a multicavity klystron. 287
- Figure 6.22** Beam-current variation as a function of modulating-anode voltage. 288
- Figure 6.23** The effect of a magnetic field on the electron beam of a klystron. 288
- Figure 6.24** Field pattern of a klystron electromagnet. 289
- Figure 6.25** Field pattern and beam shape in a properly adjusted magnetic field. 289
- Figure 6.26** Distortion of the field pattern and beam shape due to magnetic material in the magnetic field. 290
- Figure 6.27** Klystron cavity: (*a*) physical element, (*b*) equivalent electric circuit. 290
- Figure 6.28** Capacitance-tuned klystron cavity: (*a*) physical element, (*b*) equivalent circuit. 291
- Figure 6.29** Schematic equivalent circuit of a four-cavity klystron. 292
- Figure 6.30** Klystron loop coupling: (*a*) mechanical arrangement, (*b*) equivalent electric circuit. 292
- Figure 6.31** Plot of the relative phase of the reference electrons as a function of axial distance in a high-efficiency klystron. 293
- Figure 6.32** Plot of the normalized RF beam currents as a function of distance along the length of a high-efficiency klystron. 293
- Figure 6.33** Typical gain, output power, and drive requirements for a klystron. 294
- Figure 6.34** Klystron beam current as a function of annular control electrode voltage. 297
- Figure 6.35** Block diagram of a switching mod-anode pulser. 297
- Figure 6.36** Mechanical design of the multistage depressed collector assembly. Note the “V” shape of the 4-element system. 301
- Figure 6.37** A partially assembled MSDC collector. 302
- Figure 6.38** Beam current as a function of annular control electrode voltage for an MSDC klystron. 302
- Figure 6.39** Collector electron trajectories for the carrier-only condition. Note that nearly all electrons travel to the last electrode (4), producing electrode current  $I_4$ . 303

- Figure 6.40** Collector trajectories at 25 percent saturation. With the application of modulation, the electrons begin to sort themselves out. 303
- Figure 6.41** Collector electron trajectories at 50 percent saturation, approximately the blanking level. The last three electrodes (2, 3, and 4) share electrons in a predictable manner, producing currents  $I_2$ ,  $I_3$ , and  $I_4$ . 304
- Figure 6.42** Collector trajectories at 90 percent saturation, the sync level. Note the significant increase in the number of electrons attracted to the first electrode, producing  $I_1$ . 304
- Figure 6.43** The distribution of electrode current as a function of drive power. Note the significant drop in  $I_4$  as drive power is increased.  $I_5$  is the electrode at cathode potential. 305
- Figure 6.44** The MSDC collector assembly with the protective shield partially removed. 306
- Figure 6.45** Mechanical construction of an external-cavity MSDC tube: (a) device, (b) device in cavity assembly. 306
- Figure 6.46** Parallel configuration of the MSDC power supply. Each supply section has an output voltage that is an integral multiple of 6.125 kV. 307
- Figure 6.47** Series configuration of the MSDC power supply, which uses four identical 6.125 kV power supplies connected in series to achieve the needed voltages. 308
- Figure 6.48** Device bandwidth as a function of frequency and drive power. Beam voltage is 24.5 kV, and beam current is 5.04 A for an output power of 64 kW. These traces represent the full-power test of the MSDC device. 309
- Figure 6.49** Device bandwidth in the beam-pulsing mode as a function of frequency and drive power. Beam voltage is 24.5 kV, and beam current is 3.56 A with an output power of 34.8 kW. 309
- Figure 6.50** Simplified block diagram of a 60 kW (TVT) MSDC transmitter. The aural klystron may utilize a conventional or MSDC tube at the discretion of the user. 311
- Figure 6.51** Simplified schematic diagram of the power supply for an MSDC klystron transmitter. A single high-voltage transformer with multiple taps is used to provide the needed collector voltage potentials. 311
- Figure 6.52** Simplified schematic diagram of the Klystrode tube. 313
- Figure 6.53** A 60 kW Klystrode tube mounted in its support stand with the output cavity attached. 313
- Figure 6.54** A close-up view of the double-tuned output cavity of a 60 kW Klystrode tube. 314
- Figure 6.55** Overall structure of the IOT gun and output cavity. 315
- Figure 6.56** Pyrolytic graphite grid: (a) shell, (b) grid blank, (c) grid cut. 316
- Figure 6.57** IOT input cavity. 317
- Figure 6.58** IOT output cavity. 318
- Figure 6.59** Simplified block diagram of the crowbar circuit designed into the Klystrode SK-series (Comark) transmitters. The circuit is intended to protect the tube from potentially damaging fault currents. 319
- Figure 6.60** Schematic overview of the MSDC IOT or *constant efficiency amplifier*. 320
- Figure 6.61** Calculated efficiency of an MSDC IOT compared to an unmodified IOT. 322
- Figure 6.62** Basic elements of a traveling wave tube. 323

- Figure 6.63** Magnetic focusing for a TWT: (a) solenoid-type, (b) permanent-magnet-type, (c) periodic permanent-magnet structure. 324
- Figure 6.64** Helix structures for a TWT: (a) ring-loop circuit, (b) ring-bar circuit. 325
- Figure 6.65** Coupled-cavity interaction structures: (a) forward fundamental circuit or “cloverleaf,” (b) single-slot space harmonic circuit. 326
- Figure 6.66** Generic TWT electron gun structure. 327
- Figure 6.67** Cross-sectional view of a TWT electron gun with a curved hot cathode. 328
- Figure 6.68** Generic configuration of a traveling wave tube. 328
- Figure 6.69** Cross-sectional view of various collector configurations for a TWT. 329
- Figure 6.70** Power supply configuration for a multistage depressed collector TWT. 330
- Figure 6.71** Linear injected-beam microwave tube. 332
- Figure 6.72** Reentrant emitting-sole crossed-field amplifier tube. 333
- Figure 6.73** Conventional magnetron structure. 334
- Figure 6.74** Cavity magnetron oscillator: (a) cutaway view, (b) cross section view perpendicular to the axis of the cathode. 335
- Figure 6.75** Cavity magnetron oscillator anode: (a) hole-and-slot type, (b) slot type, (c) vane type. 335
- Figure 6.76** Structure of a coaxial magnetron. 336
- Figure 6.77** Structure of a tunable coaxial magnetron. 336
- Figure 6.78** Cross-sectional view of a linear magnetron. 337
- Figure 6.79** Functional schematic of the M-type radial BWO. 338
- Figure 6.80** Strap-fed devices: (a) strapped radial magnetron, (b) nonreentrant strapping of a BWO. 339
- Figure 6.81** Basic structure of a helical beam tube. 341
- Figure 6.82** Functional schematic diagram of the gyrotron: (a) single coiled helical beam gyrotron, (b) electron trajectory of double-coil helical beam gyrotron. 342
- Figure 6.83** Basic structure of the gyrokystron amplifier. 343
- Figure 6.84** Basic structure of the gyrokystron traveling wave tube amplifier. 343
- Figure 6.85** Basic structure of the gyrotron backward oscillator. 344
- Figure 6.86** Basic structure of the gyrotwystron amplifier. 344
- Figure 6.87** Basic structure of the ubitron. 346
- Figure 6.88** Functional schematic diagrams of modified klystrons: (a) laddertron, (b) twystron. 346
- Figure 6.89** Protection and metering system for a klystron amplifier. 349

#### RF Interconnection and Switching

- Figure 7.1** Skin effect on an isolated round conductor carrying a moderately high frequency signal. 356
- Figure 7.2** Semiflexible coaxial cable: (a) a section of cable showing the basic construction, (b) cable with various terminations. 358
- Figure 7.3** Magnitude and power factor of line impedance with increasing distance from the load for the case of a short-circuited receiver and a line with moderate attenuation: (a) voltage distribution, (b) impedance magnitude, (c) impedance phase. 361
- Figure 7.4** Power rating data for a variety of coaxial transmission lines: (a) 50  $\Omega$  line, (b) 75  $\Omega$  line. 364

- Figure 7.5** Effects of transmission line pressurization on peak power rating. Note that  $P'$  = the rating of the line at the increased pressure, and  $P$  = the rating of the line at atmospheric pressure. 366
- Figure 7.6** Attenuation characteristics for a selection of coaxial cables: (a) 50  $\Omega$  line, (b) 75  $\Omega$  line. 367
- Figure 7.7** Conversion chart showing the relationship between decibel loss and efficiency of a transmission line: (a) high-loss line, (b) low-loss line. 369
- Figure 7.8** The variation of coaxial cable attenuation as a function of ambient temperature. 370
- Figure 7.9** The effect of load VSWR on transmission line loss. 370
- Figure 7.10** Field configuration of the dominant or  $TE_{1,0}$  mode in a rectangular waveguide: (a) side view, (b) end view, (c) top view. 374
- Figure 7.11** Field configuration of the dominant mode in circular waveguide. 375
- Figure 7.12** Ridged waveguide: (a) single-ridged, (b) double-ridged. 376
- Figure 7.13** The effects of parasitic energy in circular waveguide: (a) trapped cross-polarization energy, (b) delayed transmission of the trapped energy. 377
- Figure 7.14** Physical construction of doubly truncated waveguide. 378
- Figure 7.15** A probe configured to introduce a reflection in a waveguide that is adjustable in magnitude and phase. 379
- Figure 7.16** Waveguide obstructions used to introduce compensating reflections: (a) inductive window, (b) capacitive window, (c) post (inductive) element. 380
- Figure 7.17** Waveguide stub elements used to introduce compensating reflections: (a) series *tee* element, (b) shunt *tee* element. 381
- Figure 7.18** Cavity resonator coupling: (a) coupling loop, (b) equivalent circuit. 383
- Figure 7.19** Filter characteristics by type: (a) low-pass, (b) high-pass, (c) bandpass, (d) bandstop. 385
- Figure 7.20** Filter characteristics by alignment, third-order, all-pole filters: (a) magnitude, (b) magnitude in decibels. 386
- Figure 7.21** The effects of filter order on rolloff (Butterworth alignment). 387
- Figure 7.22** Physical model of a 90° hybrid combiner. 388
- Figure 7.23** Operating principles of a hybrid combiner. This circuit is used to add two identical signals at inputs A and B. 389
- Figure 7.24** The effects of load VSWR on input VSWR and isolation: (a) respective curves, (b) coupler schematic. 391
- Figure 7.25** The effects of power imbalance at the inputs of a hybrid coupler. 392
- Figure 7.26** Phase sensitivity of a hybrid coupler. 392
- Figure 7.27** Nonconstant-impedance branch diplexer. In this configuration, two banks of filters feed into a coaxial tee. 393
- Figure 7.28** Band-stop (notch) constant-impedance diplexer module. This design incorporates two 3 dB hybrids and filters, with a terminating load on the isolated port. 394
- Figure 7.29** Bandpass constant-impedance diplexer. 395
- Figure 7.30** Schematic diagram of a six-module bandpass multiplexer. This configuration accommodates a split antenna design and incorporates patch panels for bypass purposes. 397
- Figure 7.31** Reverse-coupled  $\frac{1}{4}$ -wave hybrid combiner. 400
- Figure 7.32** Common RF switching configurations. 401

- Figure 7.33** Hybrid switching configurations: (a) phase set so that the combined energy is delivered to port 4, (b) phase set so that the combined energy is delivered to port 3. 401
- Figure 7.34** Additional switching and combining functions enabled by adding a second hybrid and another phase shifter to a hot switching combiner. 402
- Figure 7.35** The dielectric vane switcher, which consists of a long dielectric sheet mounted within a section of rectangular waveguide. 404
- Figure 7.36** Dielectric post waveguide phase shifter. 405
- Figure 7.37** Variable-phase hybrid phase shifter. 406
- Figure 7.38** Optical antenna feed systems: (a) lens, (b) reflector. 408
- Figure 7.39** Series-feed networks: (a) end feed, (b) center feed, (c) separate optimization, (d) equal path length, (e) series phase shifters. 409
- Figure 7.40** Types of parallel-feed networks: (a) matched corporate feed, (b) reactive corporate feed, (c) reactive stripline, (d) multiple reactive divider. 410
- Figure 7.41** The Butler beam-forming network. 410
- Figure 7.42** Basic concept of a Reggia-Spencer phase shifter. 411
- Figure 7.43** Switched-line phase shifter using *pin* diodes. 412
- Figure 7.44** Typical construction of a TR tube. 412
- Figure 7.45** Balanced duplexer circuit using dual TR tubes and two short-slot hybrid junctions: (a) transmit mode, (b) receive mode. 413
- Figure 7.46** Construction of a dissipative waveguide filter. 414
- Figure 7.47** Basic characteristics of a circulator: (a) operational schematic, (b) distributed constant circulator, (c) lump constant circulator. 415
- Figure 7.48** Output of a klystron operating into different loads through a high-power isolator: (a) resistive load, (b) an antenna system. 417
- Figure 7.49** Use of a circulator as a diplexer in TV applications. 418
- Figure 7.50** Using multiple circulators to form a multiplexer. 418

#### Cooling Considerations

- Figure 8.1** Blackbody energy distribution characteristics. 425
- Figure 8.2** Nukiyama heat-transfer curves: (a) logarithmic, (b) linear. 426
- Figure 8.3** Cooling system design for a power grid tube. 429
- Figure 8.4** The use of a chimney to improve cooling of a power grid tube. 429
- Figure 8.5** A poorly designed cooling system in which circulating air in the output compartment reduces the effectiveness of the heat-removal system. 430
- Figure 8.6** A manometer, used to measure air pressure. 430
- Figure 8.7** Cooling airflow requirements for a power grid tube. 431
- Figure 8.8** Combined correction factors for land-based tube applications. 434
- Figure 8.9** Conversion of mass airflow rate to volumetric airflow rate. 435
- Figure 8.10** Functional schematic of a water cooling system for a high-power amplifier or oscillator. 436
- Figure 8.11** Typical configuration of a water purification loop. 437
- Figure 8.12** The effect of temperature on the resistivity of ultrapure water. 438
- Figure 8.13** Vapor-phase-cooled tubes removed from their companion boilers. 441
- Figure 8.14** Vapor-phase cooling system for a power tube. 442
- Figure 8.15** Cross section of a *holed anode* design for vapor-phase cooling. 444
- Figure 8.16** A 4CV35,000A tetrode mounted in its boiler assembly. 444
- Figure 8.17** Control box for a vapor-phase cooling system. 445

- Figure 8.18** Cutaway view of a boiler and tube combination. 446
- Figure 8.19** Cutaway view of a control box. 447
- Figure 8.20** Typical four-tube vapor cooling system with a common water supply. 448
- Figure 8.21** Cutaway view of a pressure equalizer fitting. 449
- Figure 8.22** Typical four-tube vapor cooling system using “steam-out-the-bottom” boilers. 450
- Figure 8.23** Vapor cooling system incorporating a reservoir of distilled water. 451
- Figure 8.24** Cutaway view of a “steam-out-the-bottom” boiler. 452
- Figure 8.25** Airflow system for an air-cooled power tube. 457
- Figure 8.26** A manometer device used for measuring back pressure in the PA compartment of an RF generator. 458
- Figure 8.27** A typical heating and cooling arrangement for a high-power transmitter installation. Ducting of PA exhaust air should be arranged so that it offers minimum resistance to airflow. 459
- Figure 8.28** Case study in which excessive summertime heating was eliminated through the addition of a 1 hp exhaust blower to the building. 460
- Figure 8.29** Case study in which excessive back pressure to the PA cavity was experienced during winter periods, when the rooftop damper was closed. The problem was eliminated by repositioning the damper as shown. 461
- Figure 8.30** Case study in which air turbulence at the exhaust duct resulted in reduced airflow through the PA compartment. The problem was eliminated by adding a 4-ft extension to the output duct. 462
- Figure 8.31** Closed site ventilation design, with a backup inlet/outlet system. 463
- Figure 8.32** Open site ventilation design, using no air conditioner. 465
- Figure 8.33** Transmitter exhaust-collection hood. 466
- Figure 8.34** Hybrid site ventilation design, using an air conditioner in addition to filtered outside air. 467
- Figure 8.35** Results of the “foaming test” for water purity: (a) pure sample, (b) sample that is acceptable on a short-term basis, (c) unacceptable sample. 470

#### Reliability Considerations

- Figure 9.1** Example fault tree analysis diagram: (a) process steps, (b) fault tree symbols, (c) example diagram. 479
- Figure 9.2** The statistical distribution of equipment or component failures vs. time for electronic systems and devices. 481
- Figure 9.3** Distribution of component failures identified through burn-in testing: (a) steady-state high-temperature burn-in, (b) temperature cycling. 482
- Figure 9.4** The failure history of a piece of avionics equipment vs. time. Note that 60 percent of the failures occurred within the first 200 hours of service. 483
- Figure 9.5** The roller-coaster hazard rate curve for electronic systems. 484
- Figure 9.6** The effects of environmental conditions on the roller-coaster hazard rate curve. 484
- Figure 9.7** The effects of environmental stress screening on the reliability *bathtub* curve. 485
- Figure 9.8** Venn diagram representation of the relationship between flaw precipitation and applied environmental stress. 487
- Figure 9.9** Estimation of the probable time to failure from an abnormal solder joint. 488

- Figure 9.10** Proper fingerstock scoring of filament and control grid contacts on a power tube. 493
- Figure 9.11** Damage to the grid contact of a power tube caused by insufficient fingerstock pressure. 493
- Figure 9.12** The effects of filament voltage management on a thoriated-tungsten filament power tube: (a) useful life as a function of filament voltage, (b) available power as a function of filament voltage. Note the dramatic increase in emission hours when filament voltage management is practiced. 500
- Figure 9.13** The effect of klystron emitter temperature on beam current. 501
- Figure 9.14** Arc protection circuit utilizing an energy-diverting element. 503
- Figure 9.15** A new, unused 4CX15,000A tube. Contrast the appearance of this device with the tubes shown in the following figures. 506
- Figure 9.16** Anode dissipation patterns on two 4CX15,000A tubes: (a) excessive heating, (b) normal wear. 507
- Figure 9.17** Base heating patterns on two 4CX15,000A tubes: (a) excessive heating, (b) normal wear. 507
- Figure 9.18** A 4CX5000A tube that appears to have suffered socketing problems. 508
- Figure 9.19** The interior elements of a 4CX15,000A tube that had gone to air while the filament was lit. 508
- Figure 9.20** A 4CX15,000A tube showing signs of external arcing. 509
- Figure 9.21** Electrical connections for reconditioning the gun elements of a klystron. 515

#### Device Performance Criteria

- Figure 10.1** Root-mean-square (rms) voltage measurements: (a) the relationship of rms and average values, (b) the rms measurement circuit. 525
- Figure 10.2** Average voltage measurements: (a) illustration of average detection, (b) average measurement circuit. 526
- Figure 10.3** Comparison of rms and average voltage characteristics. 527
- Figure 10.4** Peak voltage measurements: (a) illustration of peak detection, (b) peak measurement circuit. 528
- Figure 10.5** Illustration of the crest factor in voltage measurements. 529
- Figure 10.6** The effects of instrument bandwidth on voltage measurements. 530
- Figure 10.7** Example of the equivalence of voltage and power decibels. 531
- Figure 10.8** Illustration of the measurement of a phase shift between two signals. 534
- Figure 10.9** Illustration of total harmonic distortion (THD) measurement of an amplifier transfer characteristic. 535
- Figure 10.10** Example of reading THD from a spectrum analyzer. 536
- Figure 10.11** Common test setup to measure harmonic distortion with a spectrum analyzer. 537
- Figure 10.12** Simplified block diagram of a harmonic distortion analyzer. 537
- Figure 10.13** Typical test setup for measuring the harmonic and spurious output of a transmitter. The notch filter is used to remove the fundamental frequency to prevent overdriving the spectrum analyzer input and to aid in evaluation of distortion components. 538
- Figure 10.14** Conversion graph for indicated distortion and true distortion. 538
- Figure 10.15** Example of interference sources in distortion and noise measurements. 539

- Figure 10.16** Transfer-function monitoring configuration using an oscilloscope and distortion analyzer. 539
- Figure 10.17** Illustration of problems that occur when measuring harmonic distortion in band-limited systems. 540
- Figure 10.18** Frequency-domain relationships of the desired signals and low-order IMD products. 541
- Figure 10.19** Test setup for measuring the intermodulation distortion of an RF amplifier using a spectrum analyzer. 542
- Figure 10.20** Typical two-tone IMD measurement, which evaluates the third-order products within the bandpass of the original tones. 543
- Figure 10.21** Illustration of the addition of distortion components: (a) addition of transfer-function nonlinearities, (b) addition of distortion components. 543
- Figure 10.22** Illustration of the cancellation of distortion components: (a) cancellation of transfer-characteristic nonlinearities, (b) cancellation of the distortion waveform. 544
- Figure 10.23** Basic model of an intermodulation correction circuit. 545
- Figure 10.24** Digital decoding process: (a) 16-QAM, (b) 8-VSB. 546
- Figure 10.25** Digitally modulated RF signal spectrum before and after amplification. 547
- Figure 10.26** RF output power variation as a function of dc beam input power for a klystron. 554
- Figure 10.27** RF output power of a klystron as a function of RF drive power. 555
- Figure 10.28** Output power variation of a klystron as a function of drive power under different tuning conditions. 556
- Figure 10.29** Ideal grid-plate transfer curve for class AB operation. 557
- Figure 10.30** Frequency spectrum of third-order IM with the interfering level equal to the carrier level. 558
- Figure 10.31** Illustration of how the VSWR on a transmission line affects the attenuation performance of the line. Scale *A* represents the VSWR at the transmitter; scale *B* represents the corresponding reflected power in watts for an example system. 561
- Figure 10.32** Illustration of how VSWR causes additional loss in a length of feedline. 562
- Figure 10.33** The generation of synchronous AM in a bandwidth-limited FM system. Note that minimum synchronous AM occurs when the system operates in the center of its passband. 564
- Figure 10.34** IPA plate-to-PA-grid matching network designed for wide bandwidth operation. 565
- Figure 10.35** Synchronous AM content of an example FM system as a function of system bandwidth. 566
- Figure 10.36** Total harmonic distortion (THD) content of an example demodulated FM signal as a function of transmission-channel bandwidth. 567
- Figure 10.37** The spectrum of an ideal AM transmitter. THD measures 0 percent; there are no harmonic sidebands. 578
- Figure 10.38** The spectrum of an ideal transmitter with the addition of IPM. 569
- Figure 10.39** Carrier amplitude regulation (carrier level shift) defined. 570
- Figure 10.40** The mechanics of intermod generation at a two-transmitter installation. 571



#### Safe Handling of Vacuum Tube Devices

**Figure 11.1** Electrocardiogram of a human heartbeat: (a) healthy rhythm, (b) ventricular fibrillation. 577

**Figure 11.2** Effects of electric current and time on the human body. Note the “let-go” range. 578

**Figure 11.3** Basic design of a ground-fault interrupter (GFI). 579

**Figure 11.4** Example of how high voltages can be generated in an RF load matching unit. 580

**Figure 11.5** Basic first aid treatment for electric shock. 581

**Figure 11.6** AC service entrance bonding requirements: (a) 120 V phase-to-neutral (240 V phase-to-phase), (b) 3-phase 208 V wye (120 V phase-to-neutral), (c) 3-phase 240 V (or 480 V) delta. Note that the main bonding jumper is required in only two of the designs. 585

**Figure 11.7** The power density limits for nonionizing radiation exposure for humans. 588

**Figure 11.8** ANSI/IEEE exposure guidelines for microwave frequencies. 590