

# Index

---

## Index Terms

## Links

<b>A</b>		
AC Mains	3	
Frequencies	3	
Voltage	3	
Acronyms. <i>See</i> Appendix		
Air Core. <i>See</i> Core Materials		
Air Gaps. <i>See</i> Magnetics		
Aliasing	66	
Ampere's Law	72	
Average Current-Mode. <i>See</i> Current-Mode		
<b>B</b>		
Ballast, Fluorescent Lighting	12	
Baluns. <i>See</i> Filters		
Bandwidth		
Large Signal vs. Small Signal	7	135
Limitations	142	
Batteries		
"C"	11	
as Loads	10	
as Sources	4	
Charging	11	
Defined	4	
Frequency Characteristics	4	
I-V Characteristics	5	
Self-Discharge	5	
Trickle Charge	11	

## Index Terms

## Links

Beads. <i>See</i> Filters		
Bipolar Transistor, Power	20	
Baker Clamp	49	
Beta	49	
Emitter-Base Zenering	49	
Leakage	49	
Pulse Current	48	
Temperature	49	
Bode Plots. <i>See Also</i> Loop		
Don't Make Sense. <i>See</i> Loop,		
Non-Minimum Phase System		
Technique	67	
Boost. <i>See</i> Topologies		
Bootstrap Winding. <i>See</i> Startup		
Buck. <i>See</i> Topologies		
Buck-Boost. <i>See</i> Topologies		
 <b>C</b>		
Calculators		
Significant Digits	59	
Capacitors	43	
Aging	45	
Aluminum Electrolytic	43	
Ceramic	44	
dV/dt	45	
Electrolytic	43	
ESR	44	191
Life	190	
Limitations	216	
Minimum Value	44	142
Selection Guide	43	
Series Connection	46	

## Index Terms

## Links

### Capacitors (*Cont.*)

Tantalum Electrolytic	43	
Temperature Effects	190	
Tolerance	44	
Types	43	
Values	44	140
Voltage Limitations	45	
X. <i>See</i> EMI		
Y. <i>See</i> EMI		

### Comparators

Hysteresis	57	174
Offsets	57	
Oscillating	174	
Output Saturation Voltage	58	

### Compensation. *See* Loop

### Complex Numbers 122

### Component

Life	190	
------	-----	--

### Compound Converters 35

When to Use Them	36	
------------------	----	--

### Conditional Stability. *See* Loops

### Continuous Conduction 20

Buck	23	
EMI	206	
Flyback	27	
Synchronous Rectification	21	

### Control Theory. *See* Loop

### Converters. *See Also* Topologies

as Loads for Other Converters	13	
-------------------------------	----	--

*See Also* Stability, Multiple Converters

### Compound. *See* Compound Converters

Continuous vs. Discontinuous	20	206
------------------------------	----	-----

## **Index Terms**

## **Links**

Converters. <i>See Also</i> Topologies ( <i>Cont.</i> )		
Current-Mode	22	
Duty Cycle Limits	18	
Efficiency. <i>See</i> Efficiency		
High-Speed Requirements	7	
Isolation	19	
Low-Noise	8	
Modules	180	191
Number of Outputs	19	
Paralleling	2	171
Quasi-Resonant. <i>See</i> Soft-Switching		
Converters		
Resonant. <i>See</i> Resonant Converters		
Soft-Switching. <i>See</i> Soft-Switching		
Converters		
Step-Down	18	
Step-Up	18	
Synchronous Rectification	20	
Voltage-Mode	22	
Core Materials	80	88
Air	81	
Curie Temperature	82	
Ferrite	81	
High Perm	89	
Losses	82	
Molyperm	81	
MPP	81	
Powdered Iron	81	
Saturation	80	
Selecting	88	
Steel Laminations	81	
Current Fed Push-Pull. <i>See</i> Topologies		

## **Index Terms**

## **Links**

Current Limiting	170		
Current-Mode	22	138	149
Average	152		
Limitations	150		
Slope Compensation	150		
Necessity Of	152		
Stability Requirement	153		
Subharmonic Oscillation	151		
<b>D</b>			
dB	121		
DC Inductor. <i>See</i> Magnetics			
Decibels	121		
Differential Amplifiers	175	176	
Error Estimate	177		
Diodes	47		
Forward Voltage	111		
Germanium	47		
MOSFET body	48		
MOSFETs as	47		
Noise	205	206	
Paralleling	47		
Reverse Recovery	47		
Reverse Recovery Time	48		
Schottky	46		
High Voltage	47		
Discontinuous Conduction	20		
Buck	23		
EMI	206		
Flyback	27		
DMMs. <i>See</i> Meters			

## **Index Terms**

## **Links**

Duty Cycle		
Limits	18	134
DVMs. <i>See</i> Meters		
<b>E</b>		
Efficiency	179	
Definition	179	
Good	180	
Improvement	189	
Measurement	63	
Modules	180	
Power Stage	179	
Electromagnetic Interference. <i>See</i> EMI		
Electronic Loads		
Minimum Input Voltage	66	
Stability	65	
EMI		
“X” Caps	214	
“Y” Caps	214	216
Buck	19	
Common Mode	201	202
Separating from Normal Mode	203	
Conducted	200	
Current Monitoring	175	
Definitions	199	
Differential Mode. <i>See</i> Normal Mode		
Diodes	48	
Effects of Topology	19	
FCC	203	
Filters. <i>See</i> Filters		
Ground vs. Return	202	
Layout. <i>See</i> Layout		

## Index Terms

## Links

### EMI (*Cont.*)

LISN	203	
Military vs. Commercial	202	
MIL-STD-461	203	
Modules	180	
Noise Estimation	218	
Normal Mode	201	202
Separating from Common Mode	203	
Origins		
Capacitive Coupling	205	
Switching Waveforms	204	
Radiated	200	
Fixes	200	
Resonant Converters	205	
Shields	200	
Material	201	
Soft-Switching Converters	205	
Spectrum	124	
VDE	203	
Error Amplifier. <i>See</i> Loop Compensation		
ESR	44	191
<b>F</b>		
Faraday's Law	72	
FCC. <i>See</i> EMI		
Feedback	168	
<i>See Also</i> Loop		
Feedthroughs. <i>See</i> Filters		
Ferrite Cores. <i>See</i> Core Materials		
Filter Pins	201	
<i>See Also</i> Filters		

## Index Terms

## Links

### Filters

“X” Caps. <i>See</i> EMI		
“Y” Caps. <i>See</i> EMI		
Component Limitations	216	
Converter Stability	222	
High Frequency	217	
Beads	217	
Feedthroughs	218	
Filter Pins	218	
Low Frequency	212	
Baluns	215	216
Commercial vs. Military	213	
Common Mode	214	
LC, Mathematics	123	125
Limitations	217	
Normal Mode	213	216
Values	214	215
Middlebrook’s Criterion	222	
Optimization	219	
Finite Element Analysis	197	
Fluorescent Tubes	12	
Flyback. <i>See</i> Topologies		
Flyback Transformer. <i>See</i> Transformers		
Forward. <i>See</i> Topologies		

## **G**

Gain Margin. <i>See</i> Loop	
Grounds. <i>See</i> Layout	

## **H**

Heatsinks	196
High-Current Resistors	42



## Index Terms

## Links

<b>I</b>	
ICs	
Temperature	191
IGBT	20
Impedance	
Input	155
Output	158
Inductance	
Leakage. <i>See</i> Leakage Inductance	
Magnetizing. <i>See</i> Magnetizing Inductance	
Inductors. <i>See Also</i> Magnetics	
Common Mode. <i>See</i> Filters, Low	
Frequency, Baluns	
Limitations	216
Input Impedance. <i>See</i> Impedance	
Instrumentation Amplifiers. <i>See</i> Differential	
Amplifiers	
Use as Isolator	169
Isolation	
Achievable Regulation	173
Requirements	19
Techniques	168
<b>J</b>	
JFETs	50
<b>K</b>	
K-Factor. <i>See</i> Loop	
<b>L</b>	
Lab supplies	2

## Index Terms

## Links

### Layout

Component Placement	212
Current Sense Transformer	210
EMI	217
Feedback Lines	211
Gate Drivers	209
Ground Islands	209
Ground Loops	208
Signal Ground vs. Power Ground	207
Single Point Ground	208
Star Ground	208

Leakage Inductance	79
in a Forward	30

LEDs	178
------	-----

LISN	203
------	-----

Logarithms	121
------------	-----

### LOOP

Bandwidth Limitations	142
Bode Plots	129
Stability	130
Compensation	138
Conditional Stability	134
Control Theory	128
Feedback. <i>See</i> Feedback	
Gain Margin	133

### Measurement

Closed Loop	143	145
Current Loop	152	
How To	146	
If Non-Inverting Pin Isn't Available	149	
Mixer Method	144	
Open Loop	136	147

## Index Terms

## Links

### LOOP (*Cont.*)

Transformer Method	144		
Multiple Converter Stability	159		
Non-Minimum Phase Systems	153		
Phase Boost	140		
Phase Margin	129	130	
How Much?	132		
Worst Case Analysis	227		
Right Half Plane Zero	133	153	
Stability			
How To	135		
Small Signal vs. Large Signal	134		
Stable	132		
Unstable	126	131	

## **M**

### Magnetics. *See Also* Transformers

Air Gaps	97		
Making your Own	102		
Minimum	101		
Selecting	100		
Ampere's Law	72		
Analogy with Electronics	75		
core Loss	104		
Dependence on Switching Frequency	106		
Core Materials. <i>See</i> Core Materials			
Core Selection	84	97	98
Core Utilization	33		
Faraday's Law	72		
Fill Factor	90		
Flux Density Calculation	84		
Flux Density Formulae	110		

## Index Terms

## Links

Magnetics. <i>See Also</i> Transformers ( <i>Cont.</i> )		
Inductance	73	
Inductor Design	83	
Isolation	116	
Layering	117	
Length per Turn	92	
Manufacturability	115	
Number of Windings	117	
Optimum Design	83	
Permeability	73	74
Potting	117	
Power Loss	92	94
Skin Depth	108	
Insulation Thickness	109	
Specifications	118	
Temperature Rise	94	
Units	74	
Winding Area	90	
Wire		
Insulation	90	
Loss	107	
Resistance	92	
Selection	90	
Magnetizing Inductance	80	114
Measurements. <i>See</i> Loop, etc., <i>or</i> Meters		
Metastability. <i>See</i> Loop, Conditional Stability		
Meters		
Accuracy vs. Precision	61	
Averaging	61	
Bandwidth	62	
Cross-Calibration	63	
Efficiency Measment	63	

## **Index Terms**

## **Links**

### Meters (*Cont.*)

Filtering	62
MOSFET Measurement	65
Probe Placement	63
Resistance	64
RMS	62

Middlebrook's Criterion. *See* Filters

MIL-HDBK-217	192
--------------	-----

### Modules

Efficiency	180
Power Rating	191
Thermal	191

Molyperm Cores. *See* Core Materials

### Monitoring

Current	175
Compensating Inductance	177
Fail Signal	178
Failure	178
LEDs	178
Negative Voltages	173
Voltage	172

MOSFETs	20
---------	----

as Rectifiers	47
Bidirectional Conduction	50
Body Diode	48
Capacitive Coupling	206
Conduction Losses	51
Gate Charge	51
Gate Resistors	52
Gate Voltage	
Maximum	52
Logic-Level	51

## **Index Terms**

## **Links**

MOSFETs ( <i>Cont.</i> )		
Losses	51	181
Measurement	65	
N-Channel vs. P-Channel	50	
Noise	205	206
Rds,on vs. Temperature	182	
Switching Losses	51	
Temperature Calculation	51	195
Thermal Runaway	191	
vs. JFETs	50	
MOVs	216	
MPP Cores. <i>See</i> Core Materials		
MTBF	191	192
<i>See Also</i> Stress Analysis		
Improving	194	
<b>N</b>		
Negative Input Impedance. <i>See</i> Impedance		
Network Analyzer	67	
Gate Waveforms	69	
Nyquist Plots	69	
Problems	130	
Step by Step Instructions	67	
Using	136	
Noise. <i>See Also</i> EMI		
Estimation	218	
Filter	10	
Line	2	
Non-Minimum Phase Systems. <i>See</i> Loop		
Nyquist Plots	69	154

## Index Terms

## Links

<b>O</b>		
Opamps		
Errors, Minimizing	54	
Gain Limitations	54	
Gain-Bandwidth	56	
Input Bias Current	54	
Input Offset Current	53	
Input Offset Voltage	53	
Phase Shift	56	145
Slew Rate	56	134
Open Loop. <i>See</i> Loop		
Optocouplers		
Use as Isolator	169	
Oscilloscopes		
Aliasing	66	
Safety	14	
Output Impedance. <i>See</i> Impedance		
Overcurrent	167	
<b>P</b>		
Permeability. <i>See</i> Magnetics		
PFM	190	
Phase Boost. <i>See</i> Loop		
Phase Margin. <i>See</i> Loop		
Poles		
at the Origin	145	
Defined	123	
Powdered Iron Cores. <i>See</i> Core Materials		
Power Good	172	
Preload	30	179
Push-Pull. <i>See</i> Topologies		

## Index Terms

## Links

PWMS		
Problems	137	
<b>R</b>		
Reactance	75	
Reference Voltages	173	
Regulation	173	
Reliability. <i>See</i> Worst Case Analysis		
Reluctance	75	
Remanence	75	
Resistors		
Carbon Comp	38	
Maximum Value	38	142
Power Rating	39	
Pulse Power	40	
Ratios, Selecting	39	
Rheostat	40	
Selection Guide	38	
Shunts	42	
Temperature Coefficient	39	
Tolerance	39	
Trace, Using as	43	207
Types	38	
Values	38	
Voltage Rating	39	
Wire-Wound	38	
Non-Inductive	38	42
Resonant Converters	33	
EMI	205	
Why Not To Use Them	34	
Rheostats	40	
RHPZ. <i>See</i> Loop, Right Half Plane Zero		



## Index Terms

## Links

Right Half Plane Zero. *See* Loop

### S

Safety	13	
Lab	15	
Oscilloscope	14	
Saturation. <i>See</i> Core Materials		
Schottky Diodes. <i>See</i> Diodes		
Sequencing	168	
Shoot-Through	21	
Short		
Hard vs. Soft	170	
Shunts	42	
Compensating Inductance	177	
Using	64	175
Simulations	161	227
Monte Carlo	228	
Sensitivity Analysis	228	
Skin Depth. <i>See</i> Magnetics		
Slow Start. <i>See</i> Soft Start		
Soft Start	167	
Circuit	168	
Soft-Switching Converters	33	
EMI	205	
Why You Should Use Them	34	
Solar Cells	6	
Stability of Converter Running From	6	
Transfer Function	128	
Stability. <i>See Also</i> Loop		
EMI Filter. <i>See</i> Filters		
Making a Converter Oscillate	2	
Multiple Converter	159	

## **Index Terms**

## **Links**

Stability. <i>See Also</i> Loop ( <i>Cont.</i> )			
System	155		
Startup	165		
Bootstrap Winding	165		
Circuits	166		
Problems	165	168	
Worst Case Analysis	226		
Steel Laminations. <i>See</i> Core Materials			
Stress Analysis	236		
Purpose	226		
Subharmonic Oscillation. <i>See</i> Current-Mode			
Supplies	2		
New vs. Old	2		
Susceptibility. <i>See</i> EMI			
Swinging Choke	30		
Switch Selection	20		
Switching Frequency	171	189	
Maximum	171		
Synchronization	171		
Limits	172		
Synchronous Rectification	21		
Shoot-Through	21	48	218
System Stability. <i>See</i> Stability			

## **T**

Telephones	11		
Model	11		
Thermal	190		
Component Life	190		
Electrical Analogy	195		
Finite Element Analysis	197		
Heatsinks	196		

## **Index Terms**

## **Links**

Thermal ( <i>Cont.</i> )	
ICs	191
Modules	191
Topologies	
Boost	26
Buck	22
Continuous Conduction	23
Discontinuous Conduction	23
Gate Drive	23
Limitations	23
Buck-Boost	28
Limitations	29
Compound Converters. <i>See</i> Compound Converters	
Flyback	
Capacitor Limitations	27
Continuous Conduction	27
Discontinuous Conduction	27
Efficiency Calculation	181
Gain Margin	133
Isolated	25
Non-Isolated	25
Number of Outputs	28
Power Limits	27
Right-Half Plane Zero. <i>See</i> Loop	
Forward	29
Leakage Inductance	30
Minimum Load	30
Use as Isolator	169
Importance of Selection of	17

<b><u>Index Terms</u></b>	<b><u>Links</u></b>	
Push-Pull	31	
Current Fed	32	
Deadtime	32	
Voltage-Fed	31	
Quasi-Resonant. <i>See</i> Soft-Switching		
Converters		
Resonant. <i>See</i> Resonant Converters		
Selection Checklist	22	
Soft-Switching. <i>See</i> Soft-Switching		
Converters		
Toroids	78	
Fill Factor	90	
Winding Limits	116	
Trace		
Using as a Resistor	43	207
Transfer Functions		
Closed Loop	126	
Composition Law	126	
Defined	126	
Nonlinear Systems	128	
Transformers. <i>See Also</i> Magnetics		
Coupling	78	
Current	113	
Placement	210	
Flyback	77	95
Fundamental Equation	96	
Forward	110	
Fundamentals	77	
Ideal	76	
Non-Idealities	78	
Optimum Design	83	
Toroids	78	

## **Index Terms**

## **Links**

Transformers. <i>See Also</i> Magnetics ( <i>Cont.</i> )		
Turns Ratio Limit	18	
Winding	76	
Transforms	124	
Fourier	124	
Laplace	124	
Transients	200	216
Type I, II & III Amplifiers	139	

## **V**

VDE. <i>See</i> EMI		
Voltage Fed Push Pull. <i>See</i> Topologies		
Voltage References	173	
Voltage-Mode	22	

## **W**

Wire		
Gauge Ratio	116	
Insulation	117	
Maximum Size	115	
Minimum Size	114	115
Selection. <i>See</i> Magnetics		
Worst Case Analysis		
How To	225	
Purpose	225	
Table Evaluation Techniques	230	
vs. RMS	227	

## **X**

X Caps. *See* EMI

## **Y**

Y Caps. *See* EMI

**Index Terms**

**Links**

**Z**

Zeroes

Defined

123